
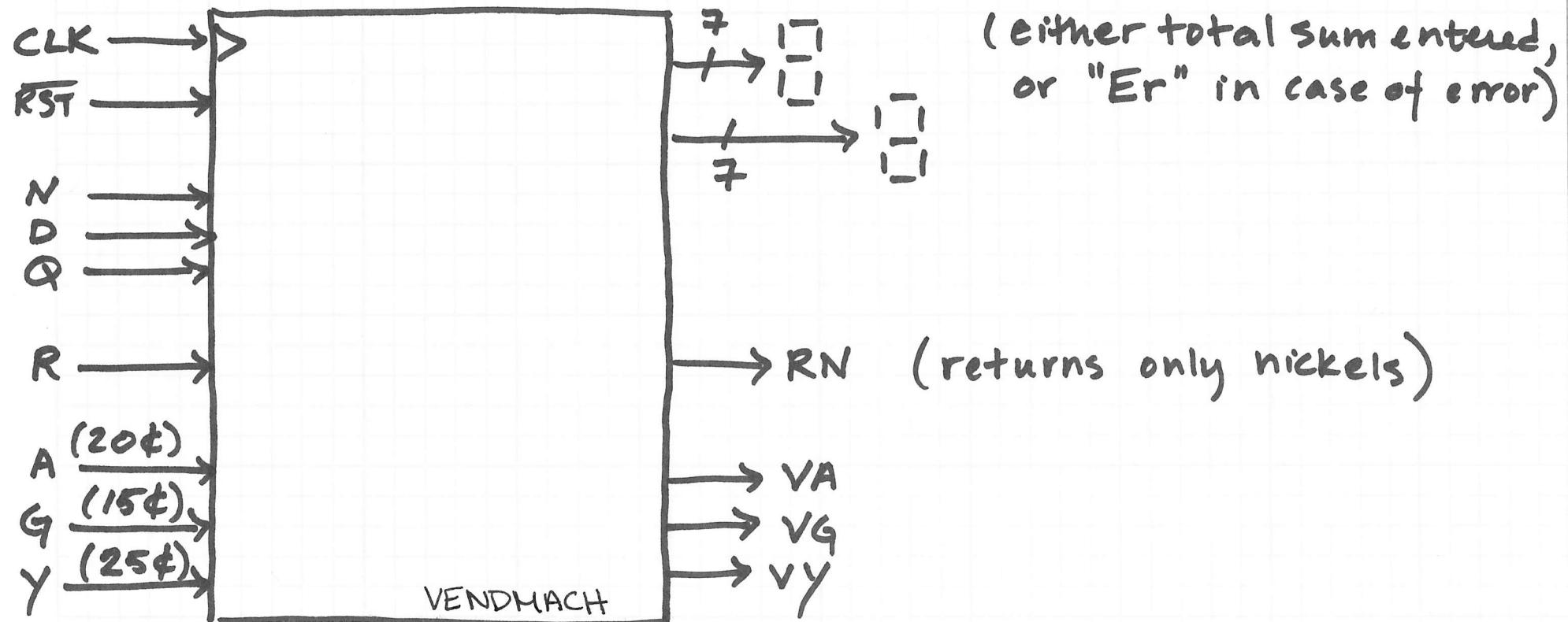


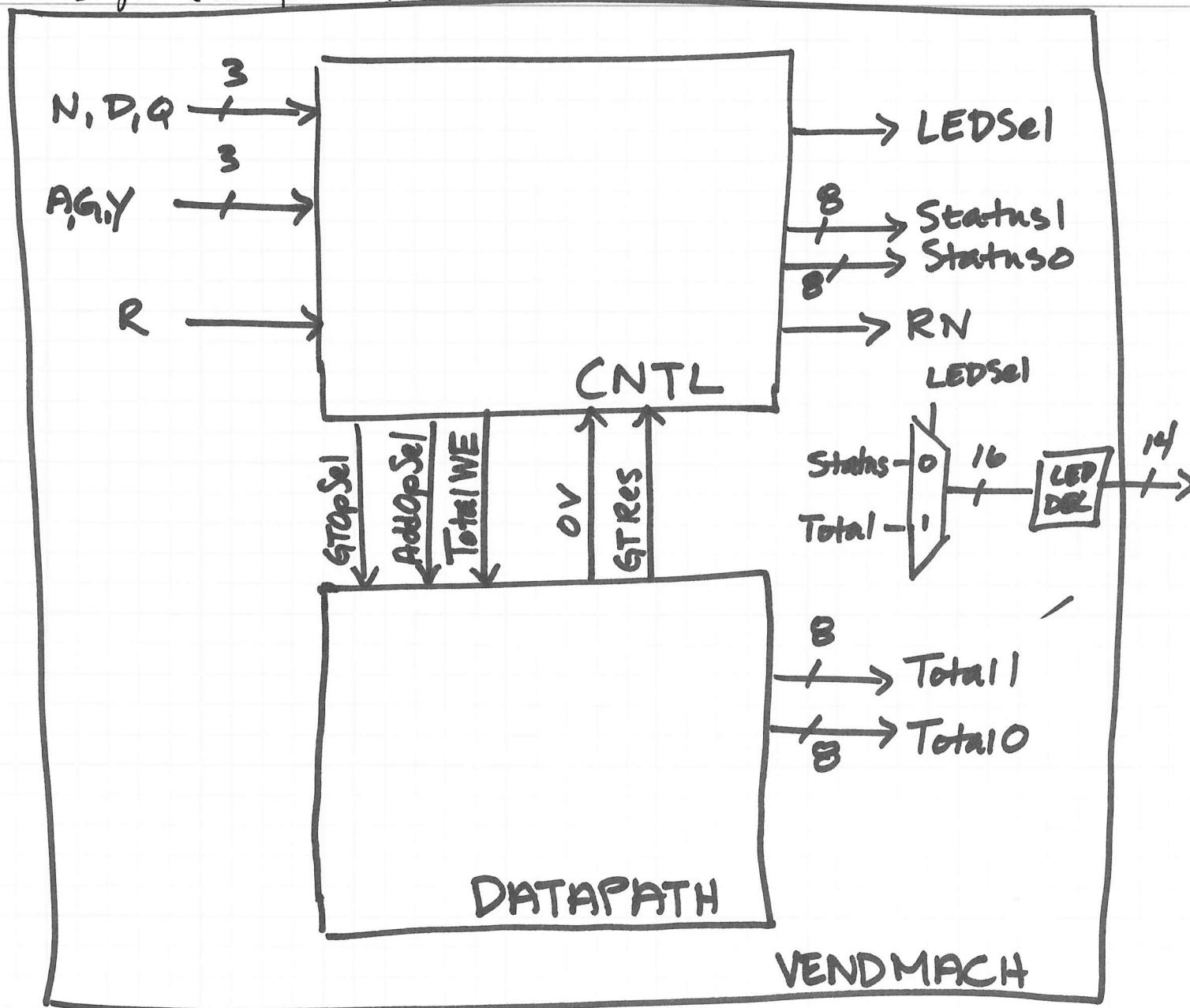
## Vending machine design exercise (3/1/10)



Two-part design: datapath + controller



Datapath intervals:

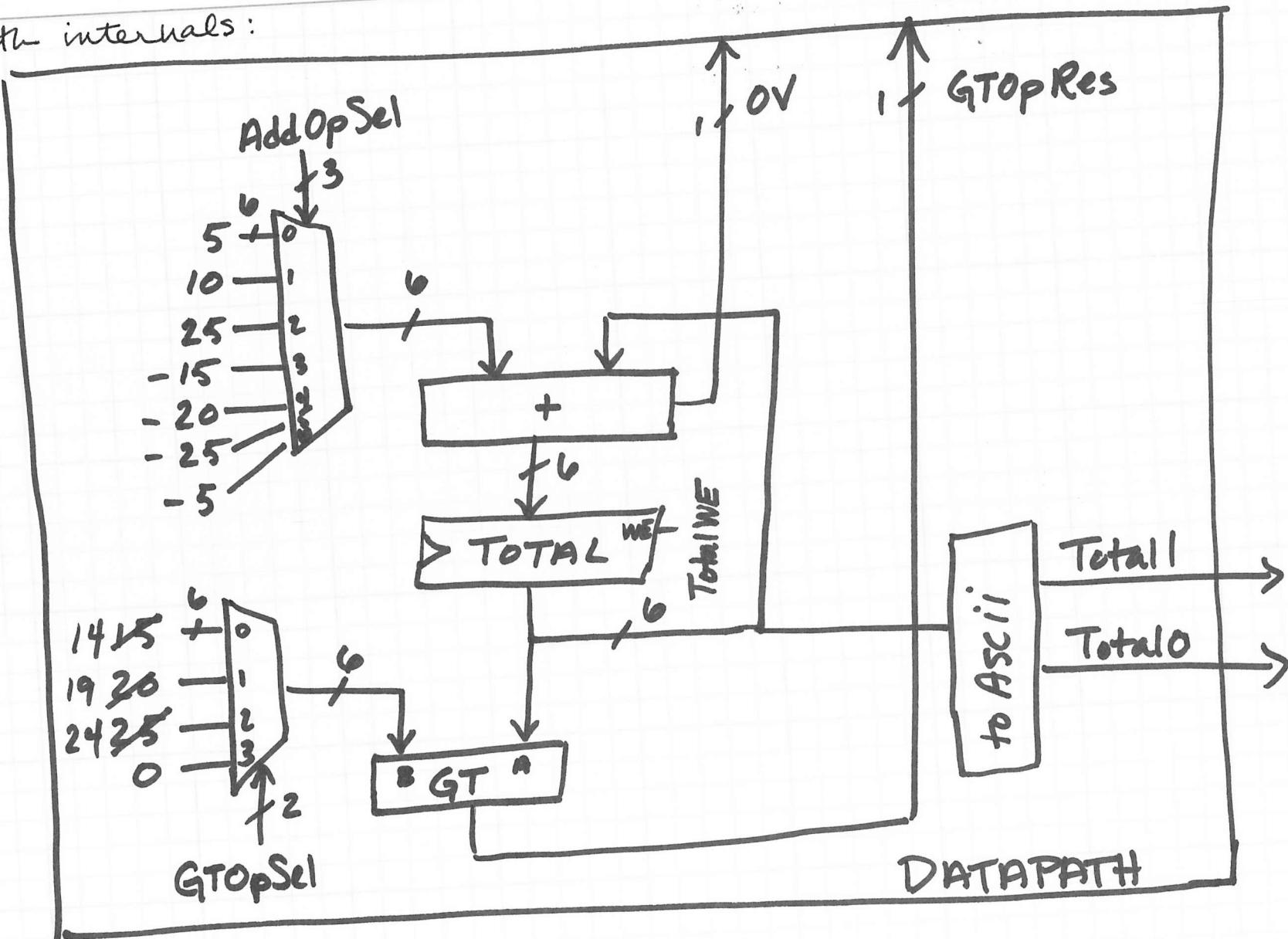

Useful expressions for user actions (simplifies control design)

$$REQA = A\bar{G}\bar{Y} \cdot NOCOIN \cdot \bar{R}$$

$$REQY = \bar{A}\bar{G}Y \cdot NOCOIN \cdot \bar{R}$$

$$REQG = \bar{A}G\bar{Y} \quad " \quad "$$

$$REQ = REQA + REQG + REQY$$

$$NOREQ = \bar{A}\bar{G}\bar{Y}$$

---

$$NICKEL = N\bar{D}\bar{Q} \cdot NOREQ \cdot \bar{R}$$

$$DIME = \bar{N}D\bar{Q} \cdot " \cdot "$$

$$QUARTER = \bar{N}\bar{D}Q \cdot " \cdot "$$

$$COIN = NICKEL + DIME + QUARTER$$

---

$$NOCOIN = \bar{N}\bar{D}\bar{Q}$$

---


$$RETURN = NOCOIN \cdot NOREQ \cdot R$$

---

$$NOACTION = NOCOIN \cdot NOREQ \cdot \bar{R}$$

legal user  
actions

control State machine:

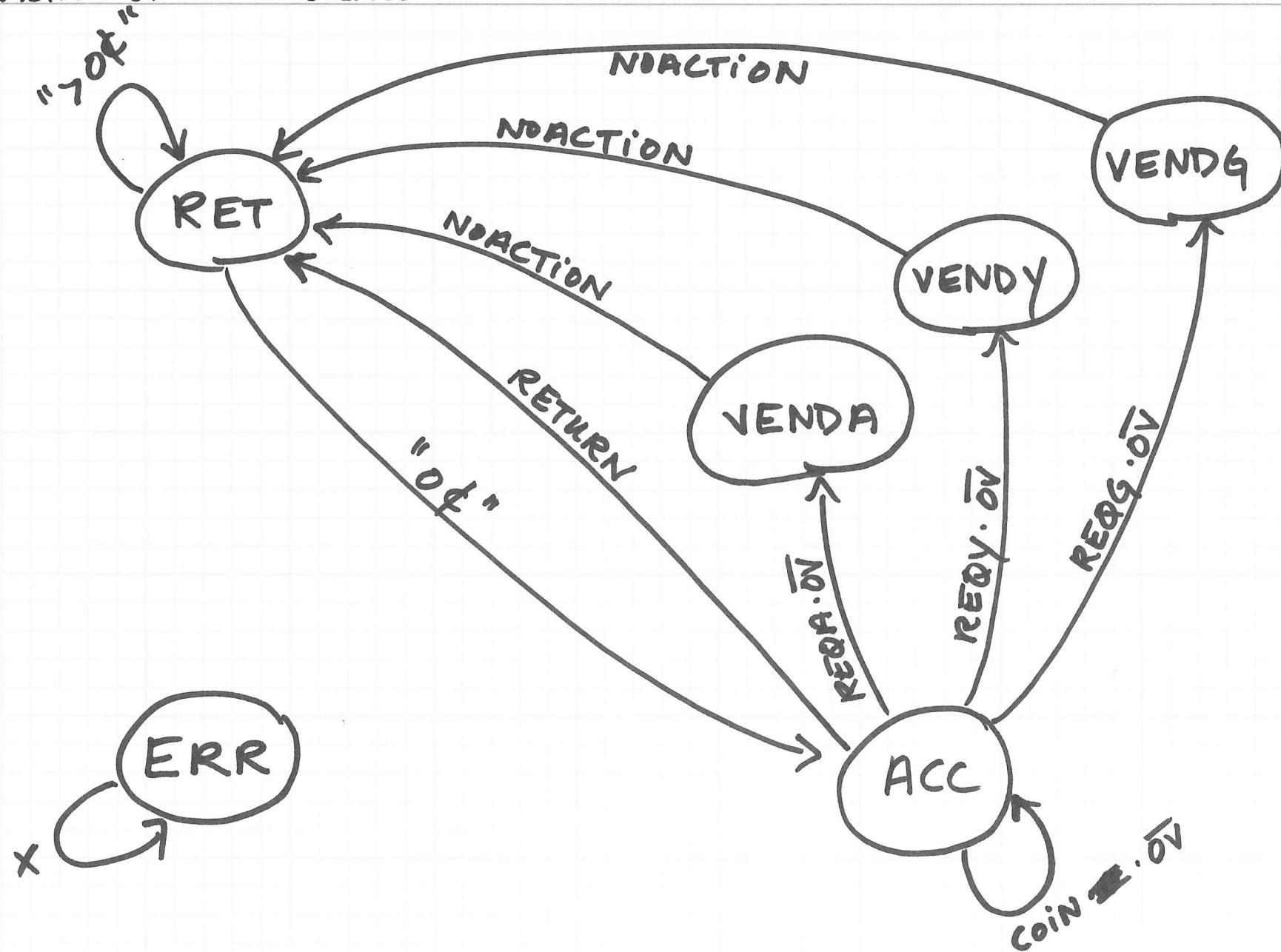

Control state table:

State	User Action	OV	GTRes	Next State	STOP Sel	Add Sel	Total WE	RN	VA, VY, VG	Status	LED Sel	D <sub>2</sub> , D <sub>1</sub> , D <sub>0</sub>
ACC	{NICKEL DIME QUARTER}	0	X	ACC	XX	{000 001 010}	1	0	000	OK	1	000
ACC	{REQA REQY REQG}	0	X	{VENDA VENDY VENDG}	01 10 00	100 101 011	1	0	000	OK	1	{001 010 011}
ACC	RETURN	0	X	RET	11	XXX	0	0	000	OK	1	100
{VENDA VENDY VENDG}	NOACTION	0	X	RET	11	XXX	0	0	{100 010 001}	OK	1	100
RET	NOACTION	0	{1 0}	{RET ACC}	11 XX	000 XXX	1 0	1 0	000	OK	1	{100 000}
ERR	X	X	X	ERR	XX	XXX	X	X	000	Err	0	111

Select State encodings:

ACC = 000 (so RST will automatically start the machine in ACC state)  
VENDA = 001  
VENDY = 010  
VENDG = 011  
RET = 100  
ERR = 111

Choose flip-flop type (D), & add "next state" signals to state table ( $D_2 D_1 D_0$ ).

Let current state be  $Q_2 Q_1 Q_0$ .

Define expressions for current state:

$$ACC = \overline{Q}_2 \overline{Q}_1 \overline{Q}_0$$

$$VENDA = \overline{Q}_2 \overline{Q}_1 Q_0$$

$$VENDY = \overline{Q}_2 Q_1 \overline{Q}_0$$

$$VENDG = \overline{Q}_2 Q_1 Q_0$$

$$RET = Q_2 \overline{Q}_1 \overline{Q}_0$$

$$ERR = Q_2 Q_1 Q_0$$

Define output signals:


$$RN = RET \cdot NOACTION \cdot \bar{OV} \cdot GTRes$$

$$VA = VENDA \cdot NOACTION \cdot \bar{OV}$$

$$VY = VENDY \cdot NOACTION \cdot \bar{OV}$$

$$VG = VENDG \cdot " \cdot "$$

$$LEDSel = \overline{ERR}$$

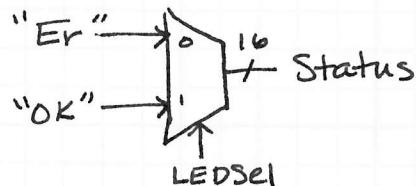

$$\text{Total WE} = ACC \cdot \bar{OV} \cdot (NICKEL + DIME + QUARTER + REQ A + REQ Y + REQ G) +$$

$$RET \cdot NOACTION \cdot \bar{OV} \cdot GTRes$$

(the above is direct from state table, but can be simplified using summary terms defined earlier.)

$$\text{Add OpSel}_2 = ACC \cdot \bar{OV} \cdot (REQ A + REQ Y)$$

$$\text{Add OpSel}_1 = ACC \cdot \bar{OV} \cdot (QUARTER + REQ G)$$

$$\text{Add OpSel}_0 = ACC \cdot \bar{OV} \cdot (DIME + REQ Y + REQ G)$$

$$GTOpSel_1 = ACC \cdot \bar{OV} \cdot (REQ Y + RETURN) + (VENDA + VENDY + VENDG) \cdot NOACTION \cdot \bar{OV} +$$

$$RET \cdot NOACTION \cdot \bar{OV} \cdot GTRes$$

$$GTOpSel_0 = ACC \cdot \bar{OV} \cdot (REQ A + RETURN) + (VENDA + VENDY + VENDG) \cdot NOACTION \cdot \bar{OV} +$$

$$RET \cdot NOACTION \cdot \bar{OV}$$

Define next state signals:

$$\overline{D_2} = ACC \cdot \overline{OV} \cdot (COIN + REQ) + RET \cdot NOACTION \cdot \overline{OV} \cdot \overline{GTR_{RES}}$$

$$\begin{aligned}\overline{D_1} &= ACC \cdot \overline{OV} \cdot (COIN + REQ_A + RETURN) + \\ &(VENDA + VENDY + VENDG + RET) \cdot NOACTION \cdot \overline{OV}\end{aligned}$$

$$\begin{aligned}\overline{D_0} &= ACC \cdot \overline{OV} \cdot (COIN + REQ_Y + RETURN) + \\ &(VENDA + VENDY + VENDG + RET) \cdot NOACTION \cdot \overline{OV}\end{aligned}$$

(Enumerate all cases in which  $D_i = 0$  because we want  
 $D_i = 1$  so that "all other" cases go to ERR.)