

CSEE 3827: Fundamentals of Computer Systems


Combinational Circuits

Outline (M&K 3.1, 3.3, 3.6-3.9, 4.1-4.2, 4.5, 9.4)

- **Combinational Circuit Design**
 - Standard combinational circuits
 - enabler
 - decoder
 - encoder / priority encoder
 - Code converter
 - MUX (multiplexer) & DeMux
 - Addition / Subtraction
 - half and full adders
 - ripple carry adder
 - carry lookahead adder
 - Shifter

Combinational circuits

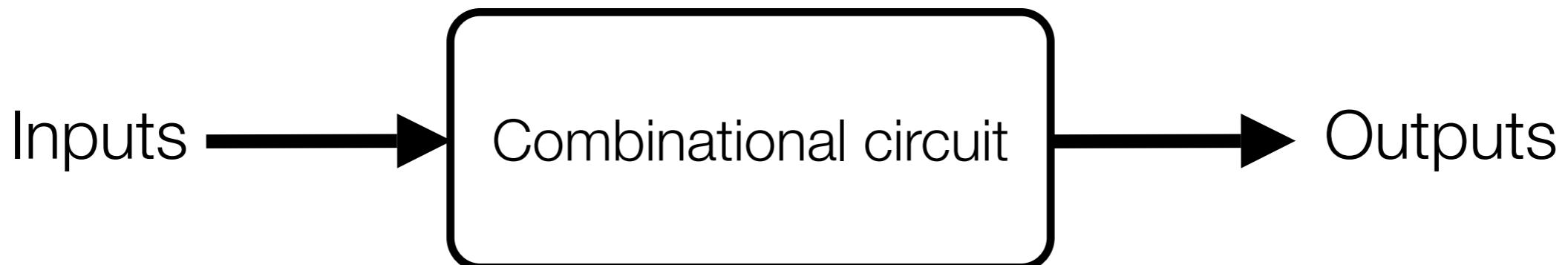
- Combinational circuits are stateless
- The outputs are functions only of the inputs



Hierarchical design


3-4

"Big" Circuit

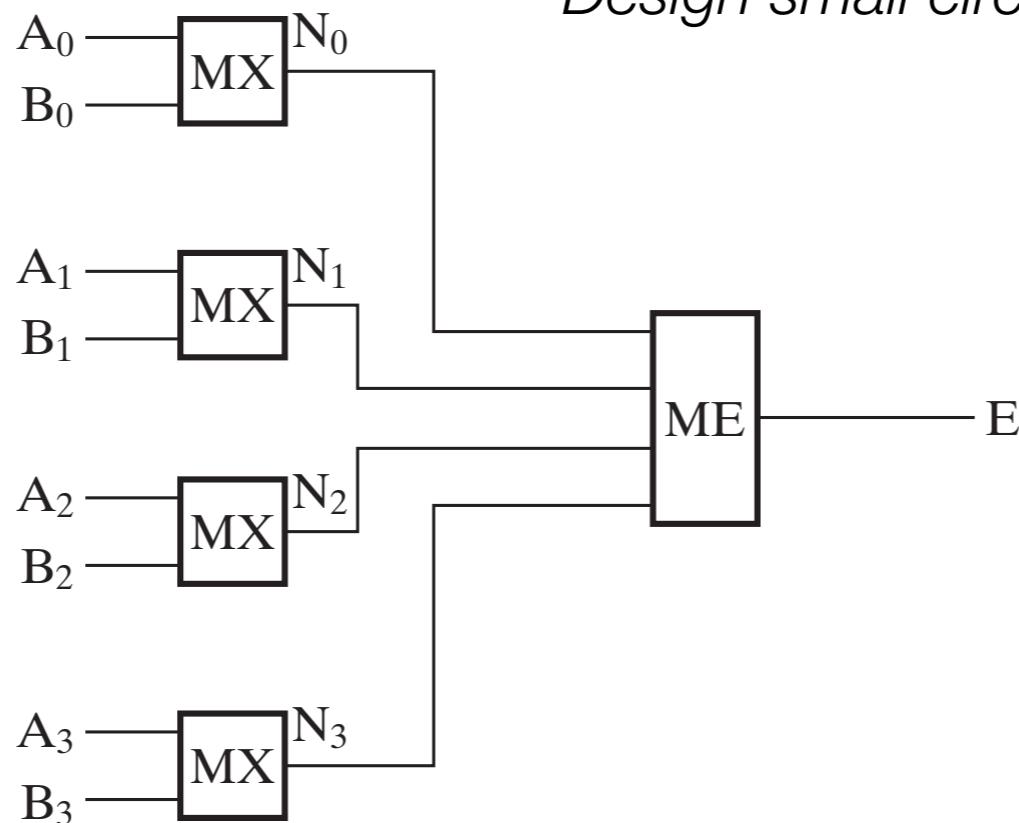


(a)

Smaller Circuits

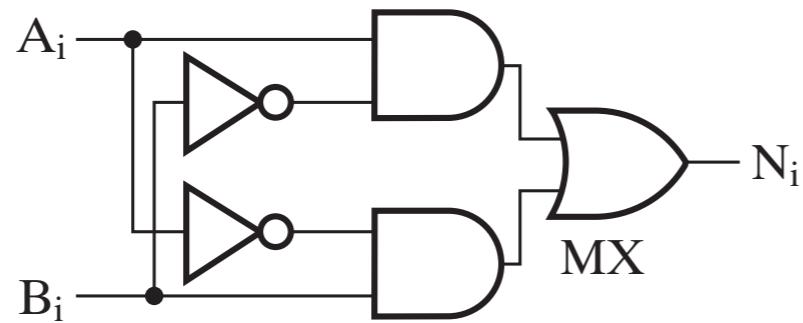

(b)

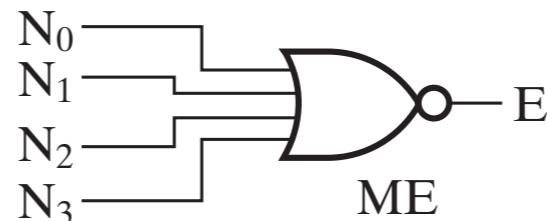


(c)

Design small circuits to be used in a bigger circuit

Enabler circuits


3-15

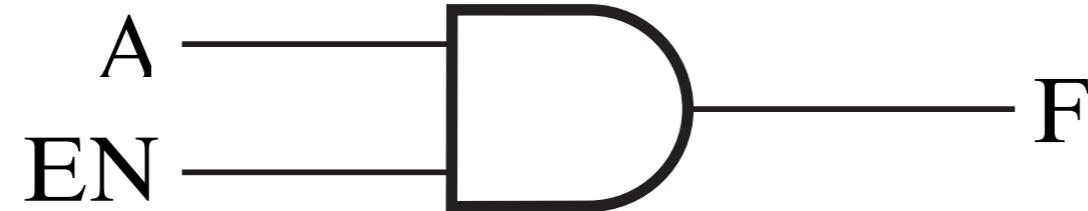Output is “enabled” ($F=X$) only when input ‘ENABLE’ signal is asserted ($EN=1$)



(a)

EN	F
0	0
1	A

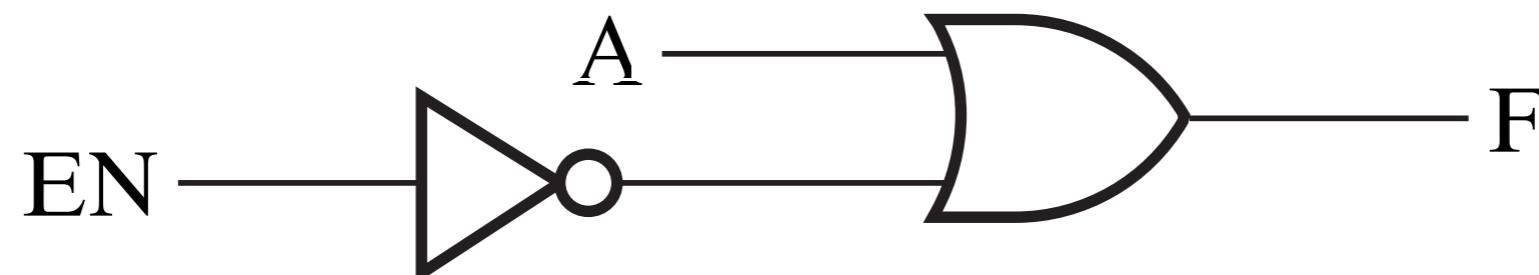


(b)

EN	F
0	1
1	A

Decoder-based circuits

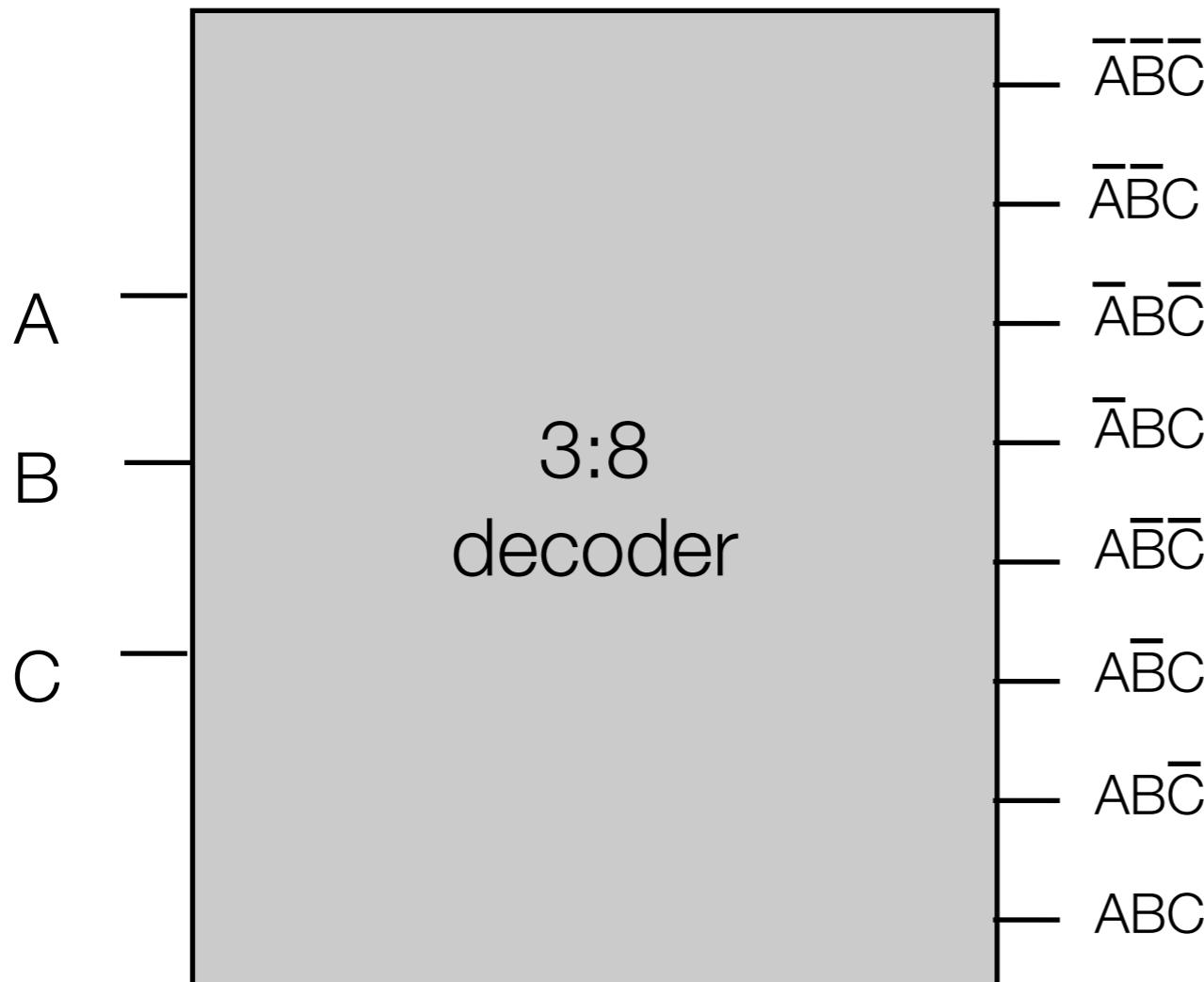
Converts n-bit input to m-bit output, where $n \leq m \leq 2^n$




*“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)*

Decoder-based circuits


So, if decoders produce minterms. . .

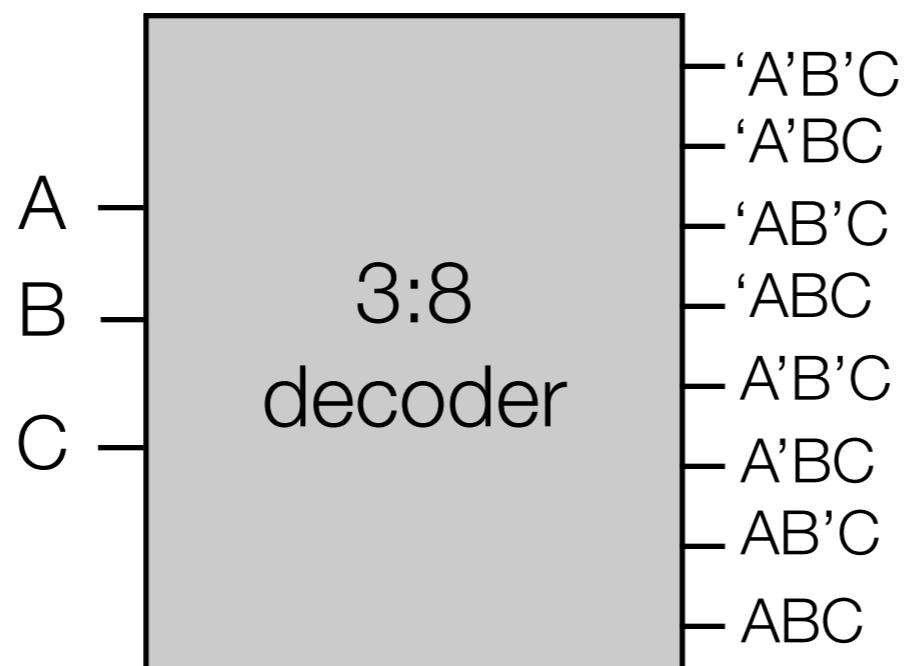


Internal design of 1:2 decoder

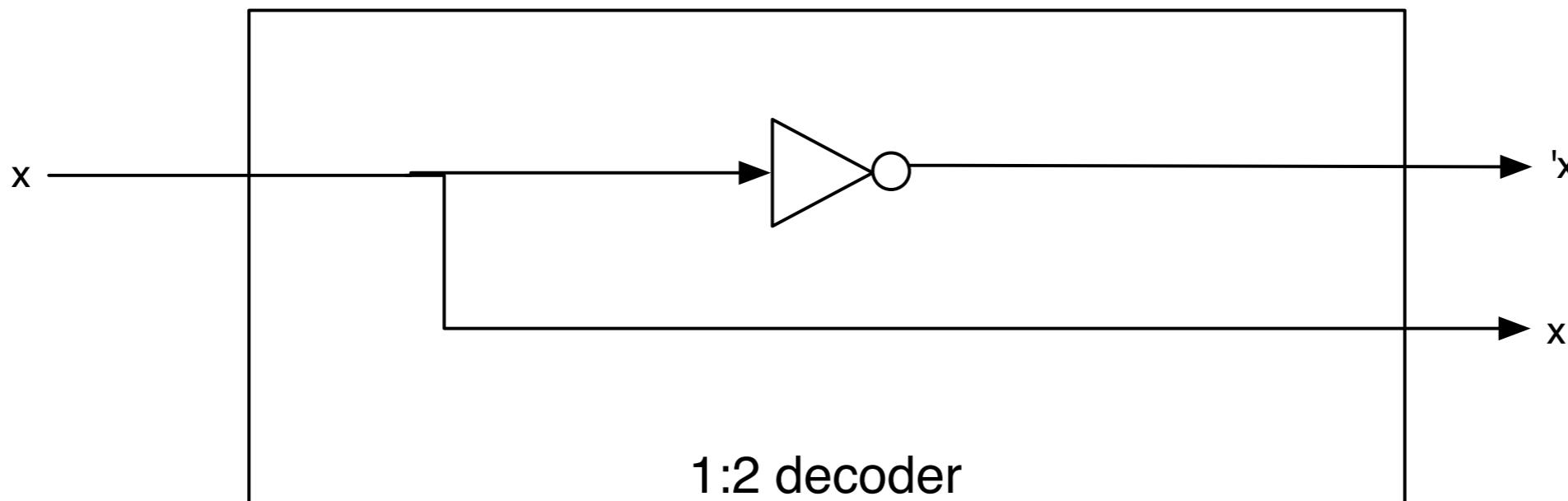

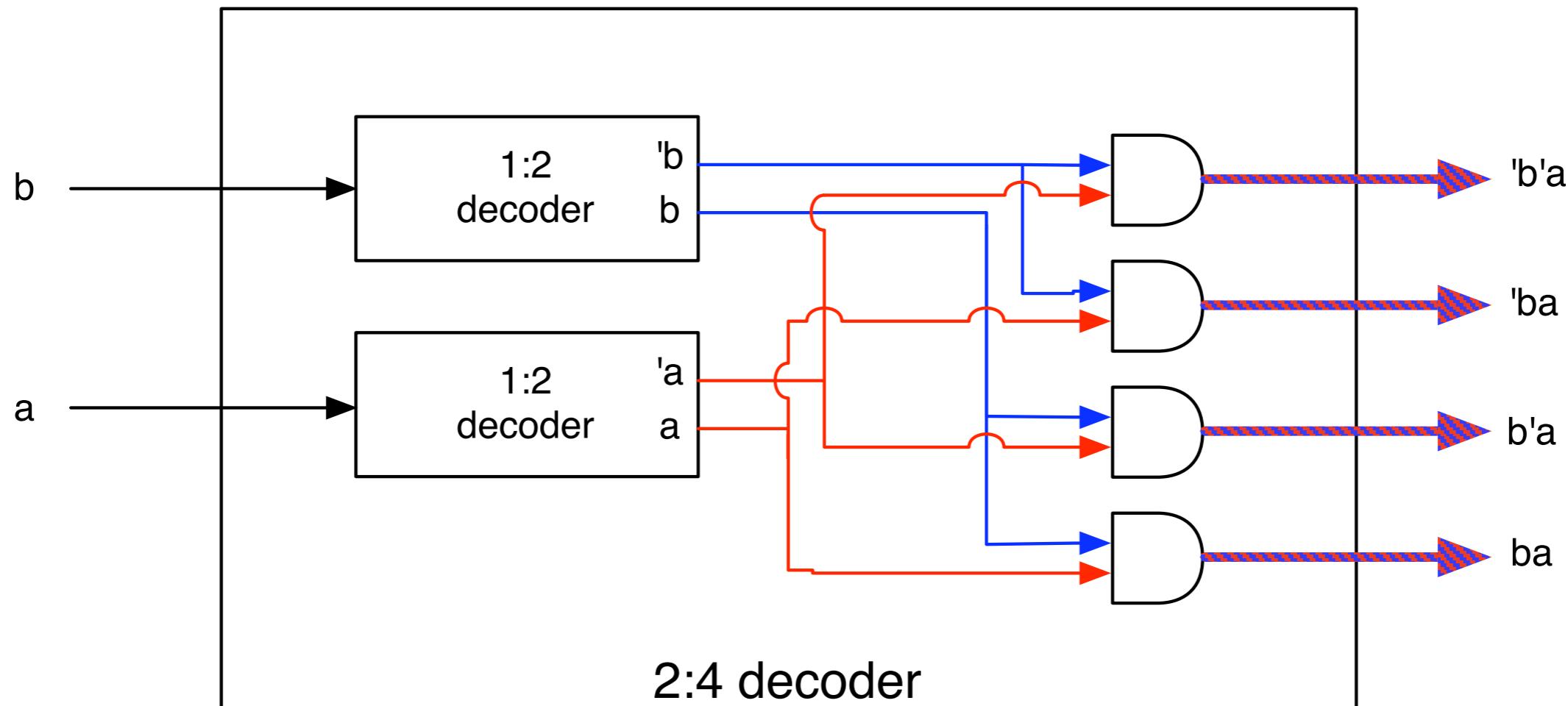Hierarchical design of decoder (2:4 decoder)



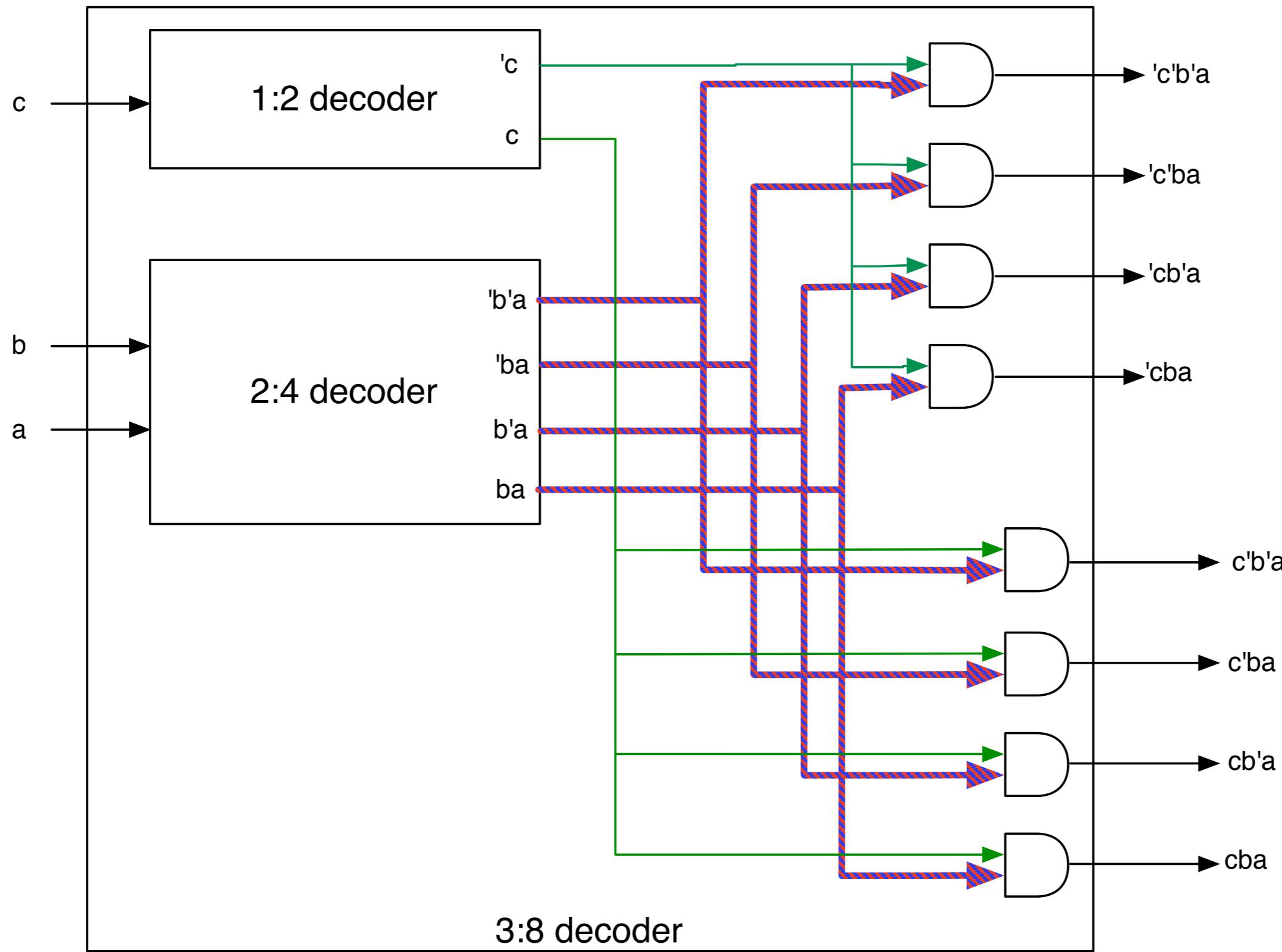Hierarchical design of decoder (3:8 decoder)



Encoders


T 3-7

Inverse of a decoder: converts m-bit input to n-bit output, where $n \leq m \leq 2^n$

 **TABLE 3-7**
Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Decoder and encoder summary

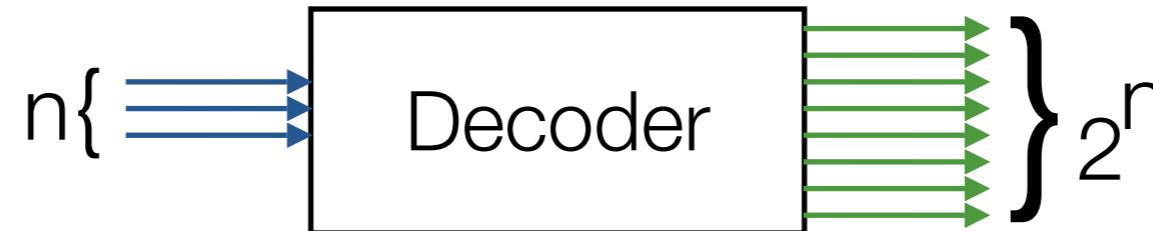

BCD values			One-hot encoding							
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



Note: for Encoders - input is assumed to be just one 1, the rest 0's

Priority Encoder

T 3-8


Like a regular encoder, but designed for any combination of inputs.

□ TABLE 3-8
Truth Table of Priority Encoder

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

General code conversion

3-3

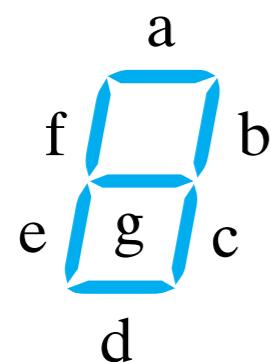


(a) Segment designation



(b) Numeric designation for display

Code conversion for the “a”

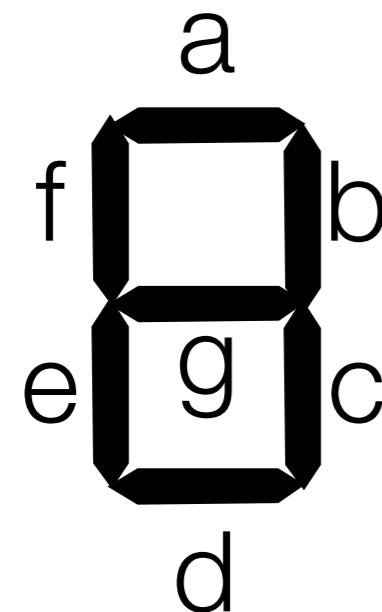


Input Output

Val	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
A	1	0	1	0	1	1	1	0	1	1	1
b	1	0	1	1	0	0	1	1	1	1	1
C	1	1	0	0	1	0	0	1	1	1	0
d	1	1	0	1	0	1	1	1	1	0	1
E	1	1	1	0	1	0	0	1	1	1	1
F	1	1	1	1	1	0	0	0	1	1	1


Multiplexers

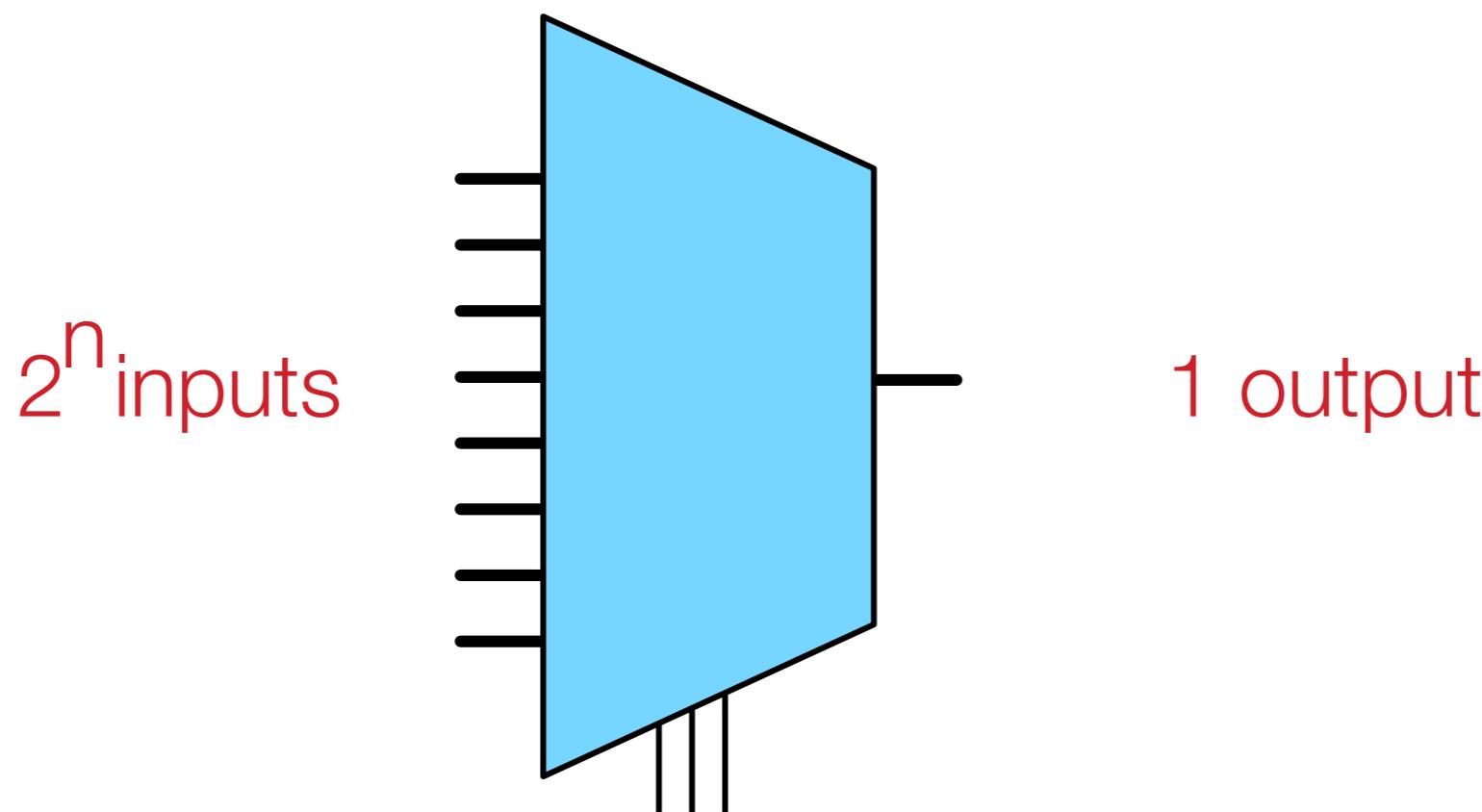- Combinational circuit that **selects** binary information from one of many input lines and directs it to one output line



2ⁿ inputs 1 output
n selection bits
indicate (in binary) which input feeds to the output


Truth table for a 4:1 mux

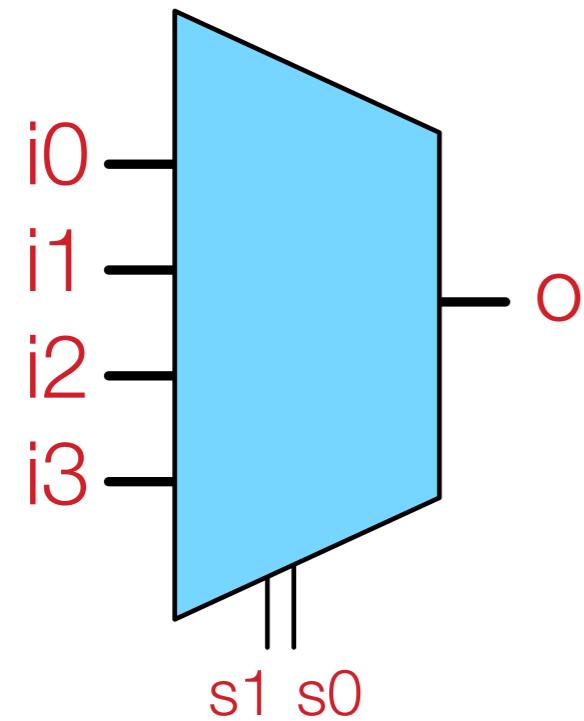

Internal mux organization


3-26

Selector Logic

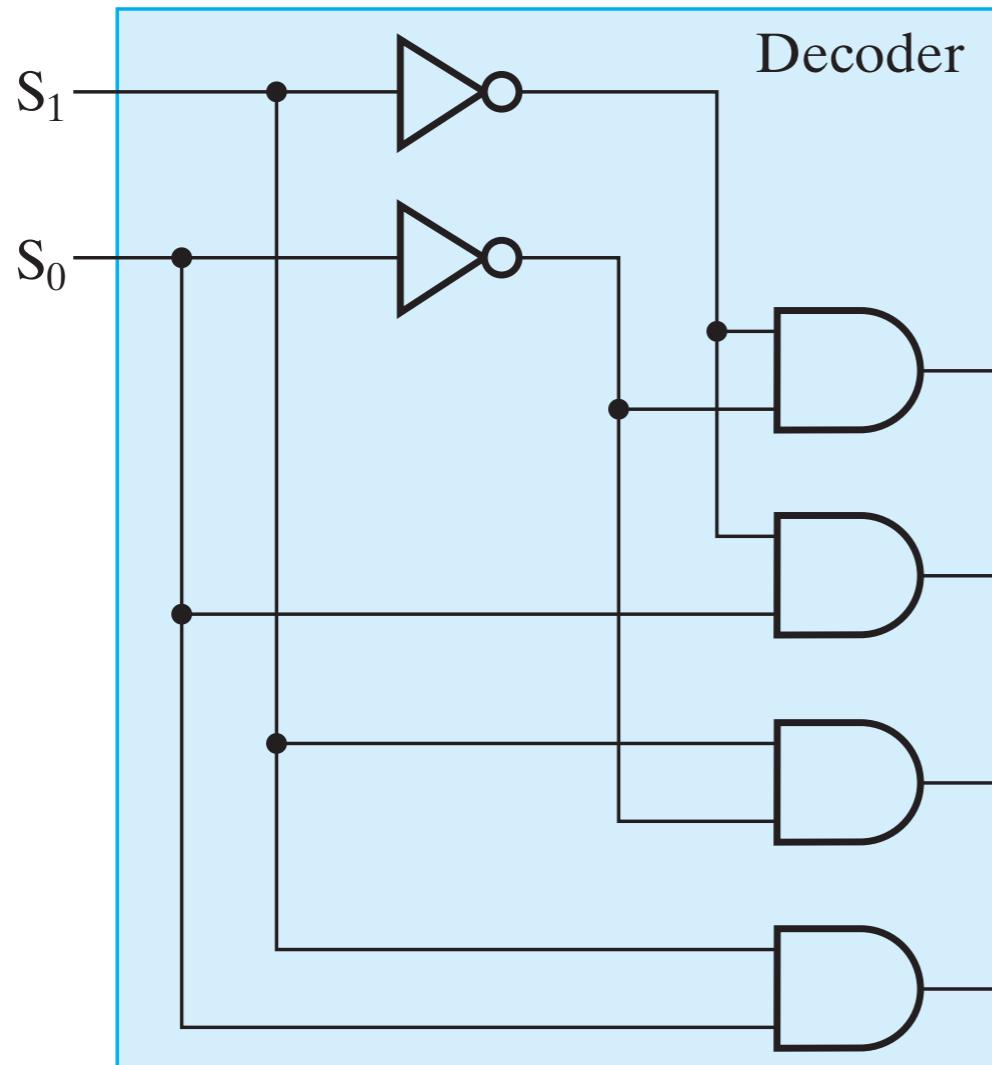

Only 1 AND gate passes “1” through

Enabler logic

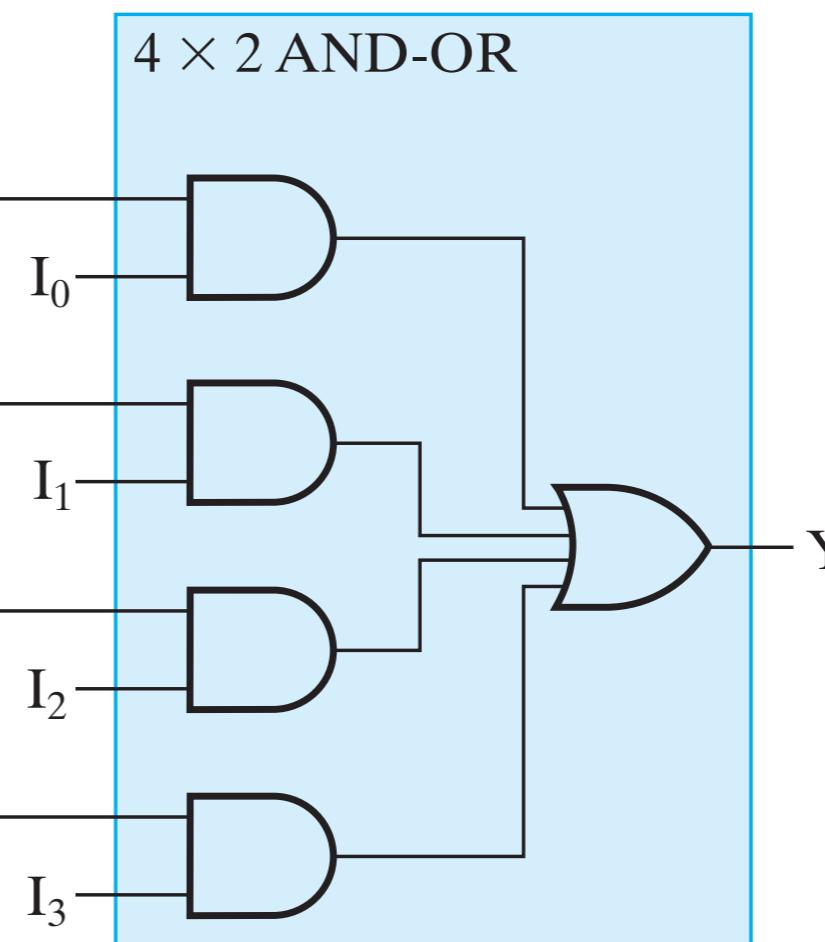


AND gates “zero out” unselected I_i

Or gate “passes through” the non-zeroed out I_i

In class exercise


How would you implement an 8:1 mux using two 4:1 muxes?

Multiplexer truth table

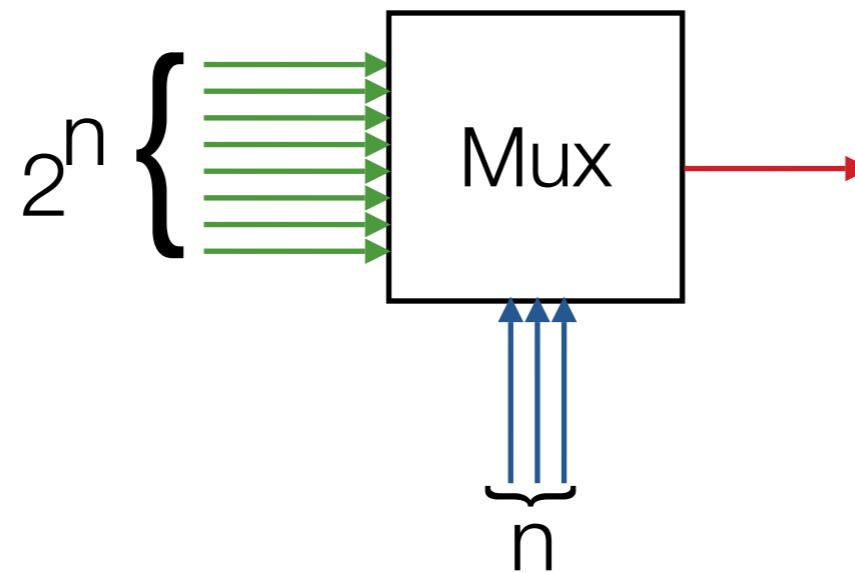


2 ⁿ inputs									n-bit BCD value			1 output
a	x	x	x	x	x	x	x	x	0	0	0	a
x	b	x	x	x	x	x	x	x	0	0	1	b
x	x	c	x	x	x	x	x	x	0	1	0	c
x	x	x	d	x	x	x	x	x	0	1	1	d
x	x	x	x	e	x	x	x	x	1	0	0	e
x	x	x	x	x	f	x	x	x	1	0	1	f
x	x	x	x	x	x	g	x	x	1	1	0	g
x	x	x	x	x	x	x	h	x	1	1	1	h

Demultiplexers

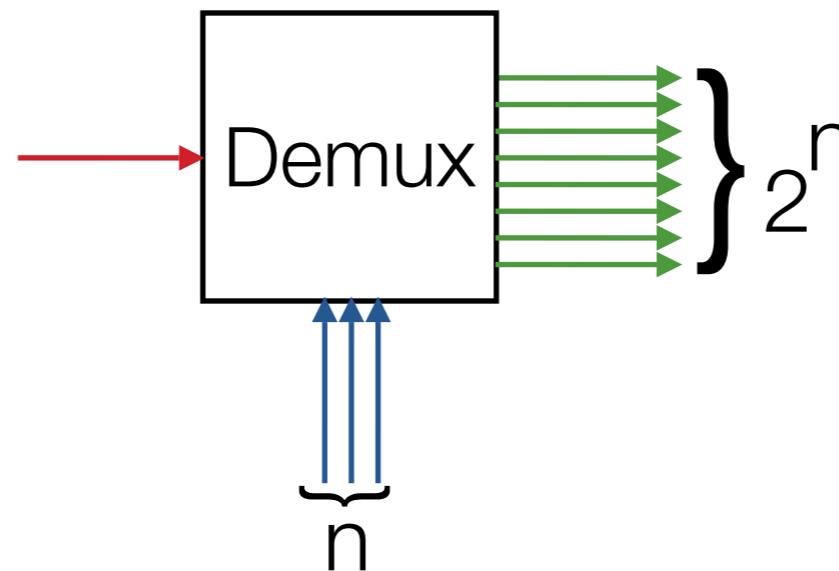

1 input	n-bit BCD value			2 ⁿ outputs							
a	0	0	0	a	0	0	0	0	0	0	0
b	0	0	1	0	b	0	0	0	0	0	0
c	0	1	0	0	0	c	0	0	0	0	0
d	0	1	1	0	0	0	d	0	0	0	0
e	1	0	0	0	0	0	0	e	0	0	0
f	1	0	1	0	0	0	0	0	f	0	0
g	1	1	0	0	0	0	0	0	0	g	0
h	1	1	1	0	0	0	0	0	0	0	h

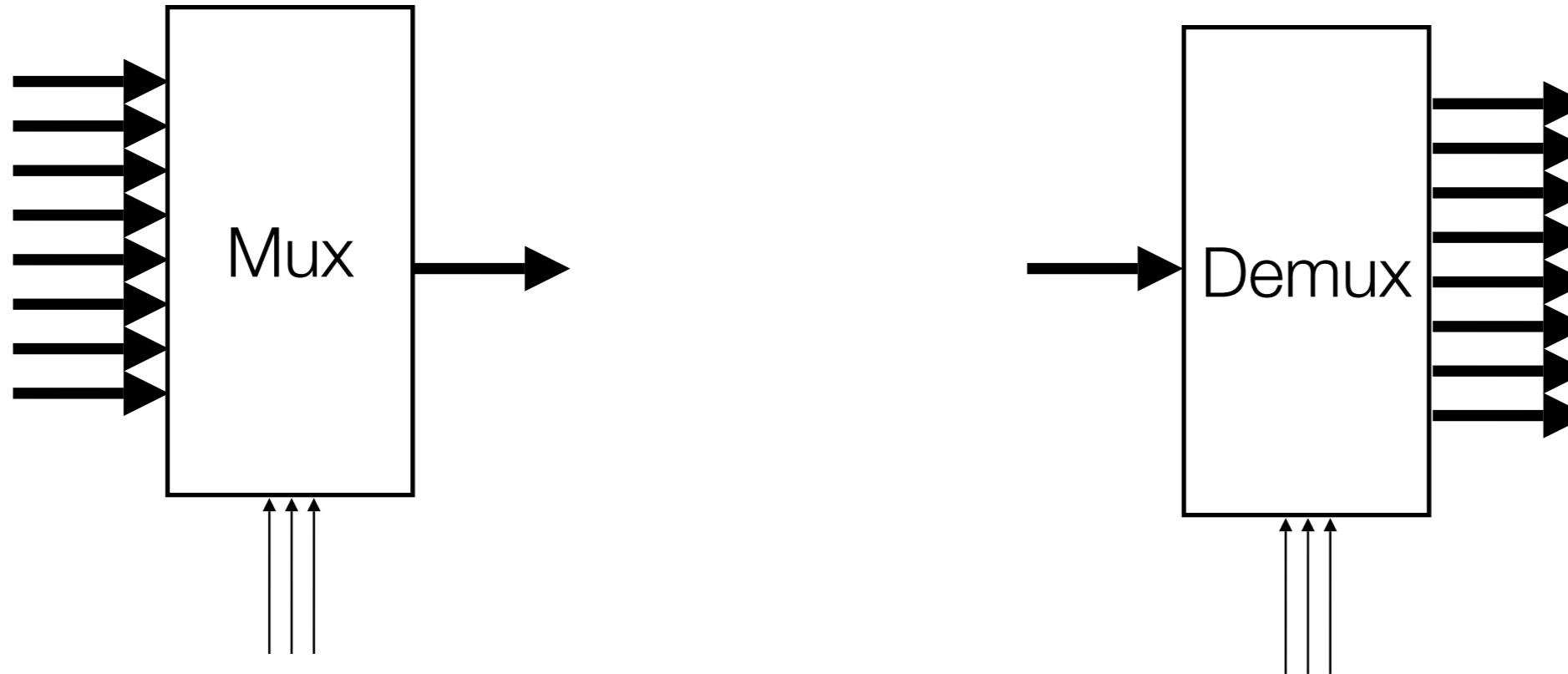Muxes and demuxes called “steering logic”




“merge”

“fork”


Decimal v. binary addition

$$\begin{array}{r} \textcolor{red}{1} \text{ } \textcolor{red}{1} \\ 4 \text{ } 3 \text{ } 5 \text{ } 8 \text{ } 2 \\ + \text{ } 2 \text{ } 2 \text{ } 5 \text{ } 7 \text{ } 3 \\ \hline \textcolor{red}{6} \text{ } 6 \text{ } 1 \text{ } 5 \text{ } 5 \end{array}$$

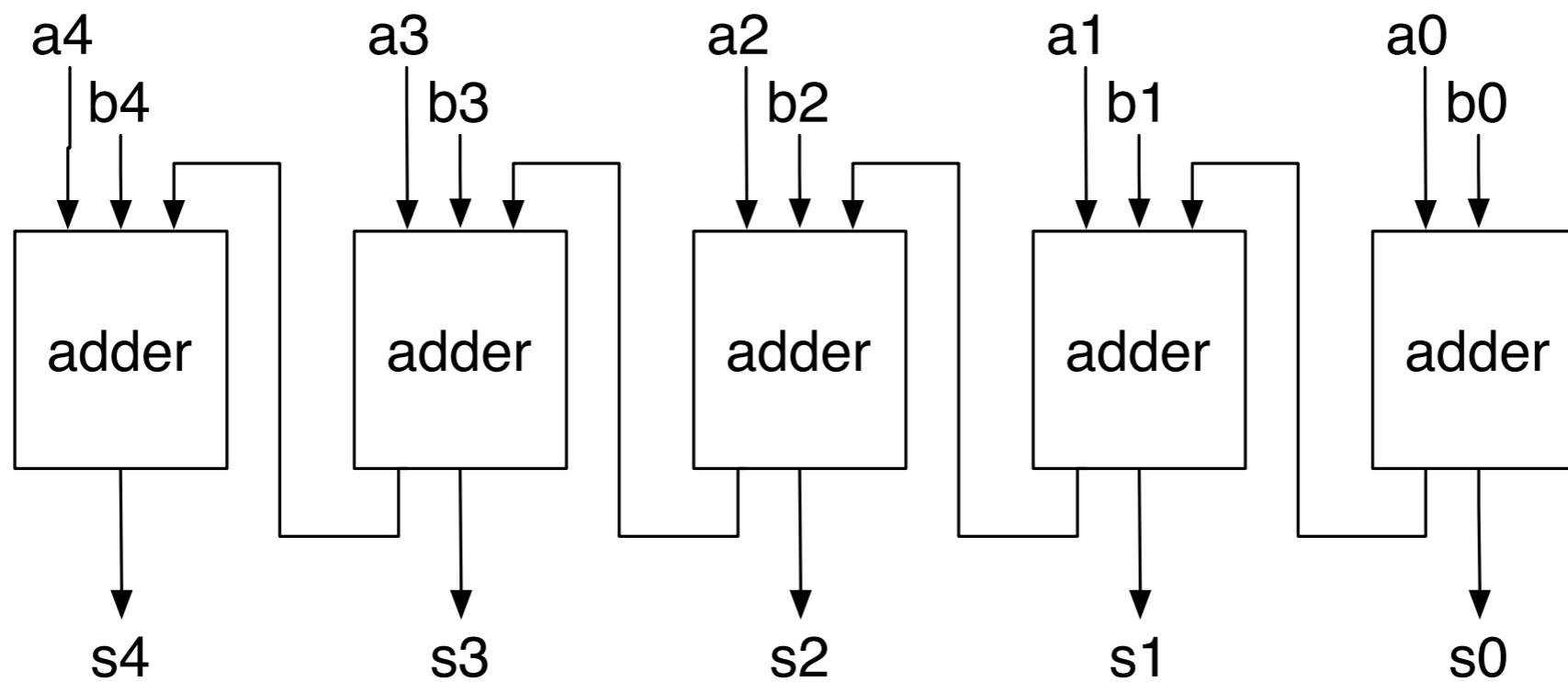
$$\begin{array}{r} \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\ 0 \text{ } 1 \text{ } 0 \text{ } 1 \text{ } 1 \\ + \text{ } 0 \text{ } 0 \text{ } 1 \text{ } 0 \text{ } 1 \\ \hline \textcolor{red}{1} \text{ } 0 \text{ } 0 \text{ } 0 \end{array}$$



Ripple carry adder

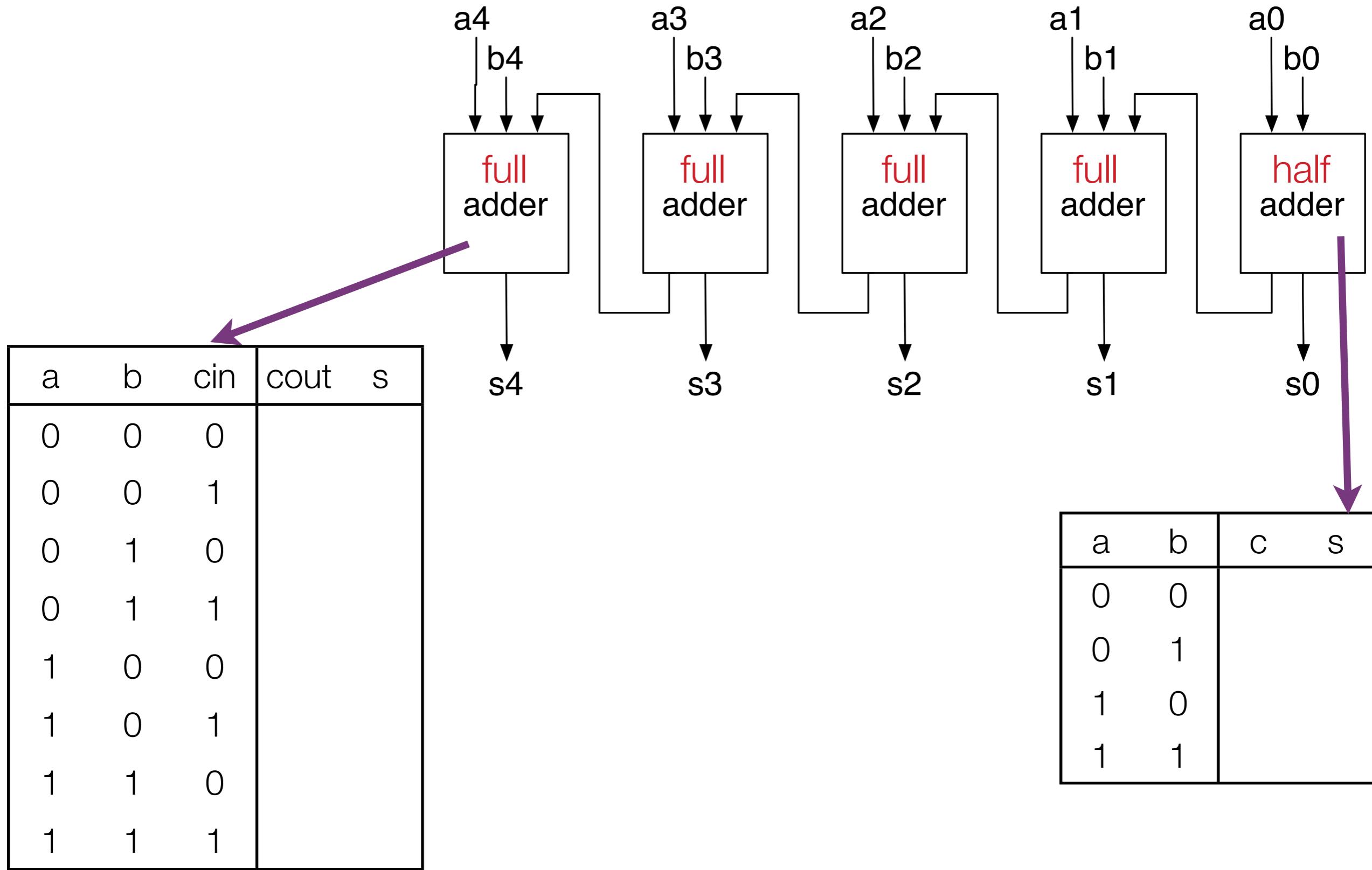

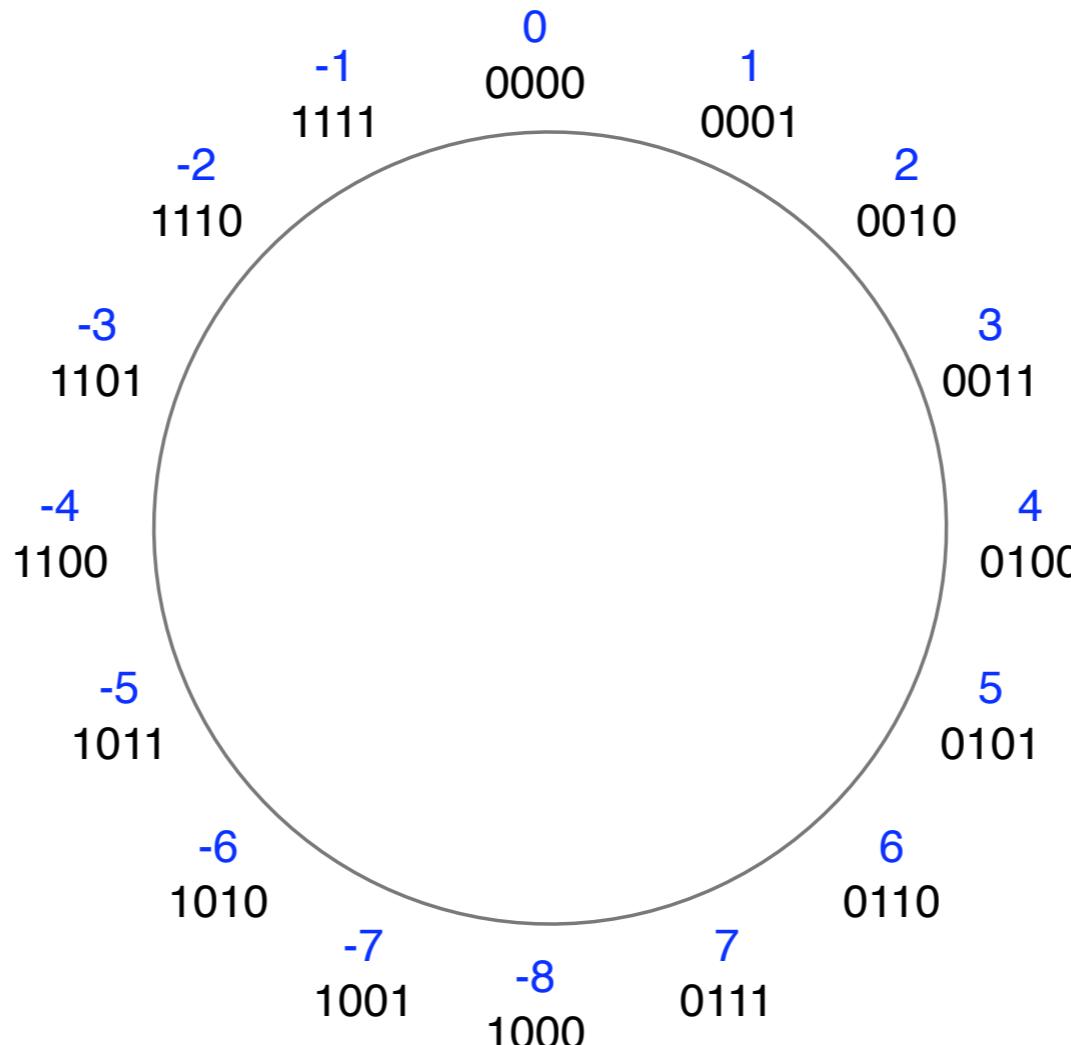Subtraction w. twos complement representation




Can be accomplished with a **twos-complementor** and an **adder**


In class exercise: designing an adder-subtractor

Adder/subtractor for #'s in 2's complement form

4-7

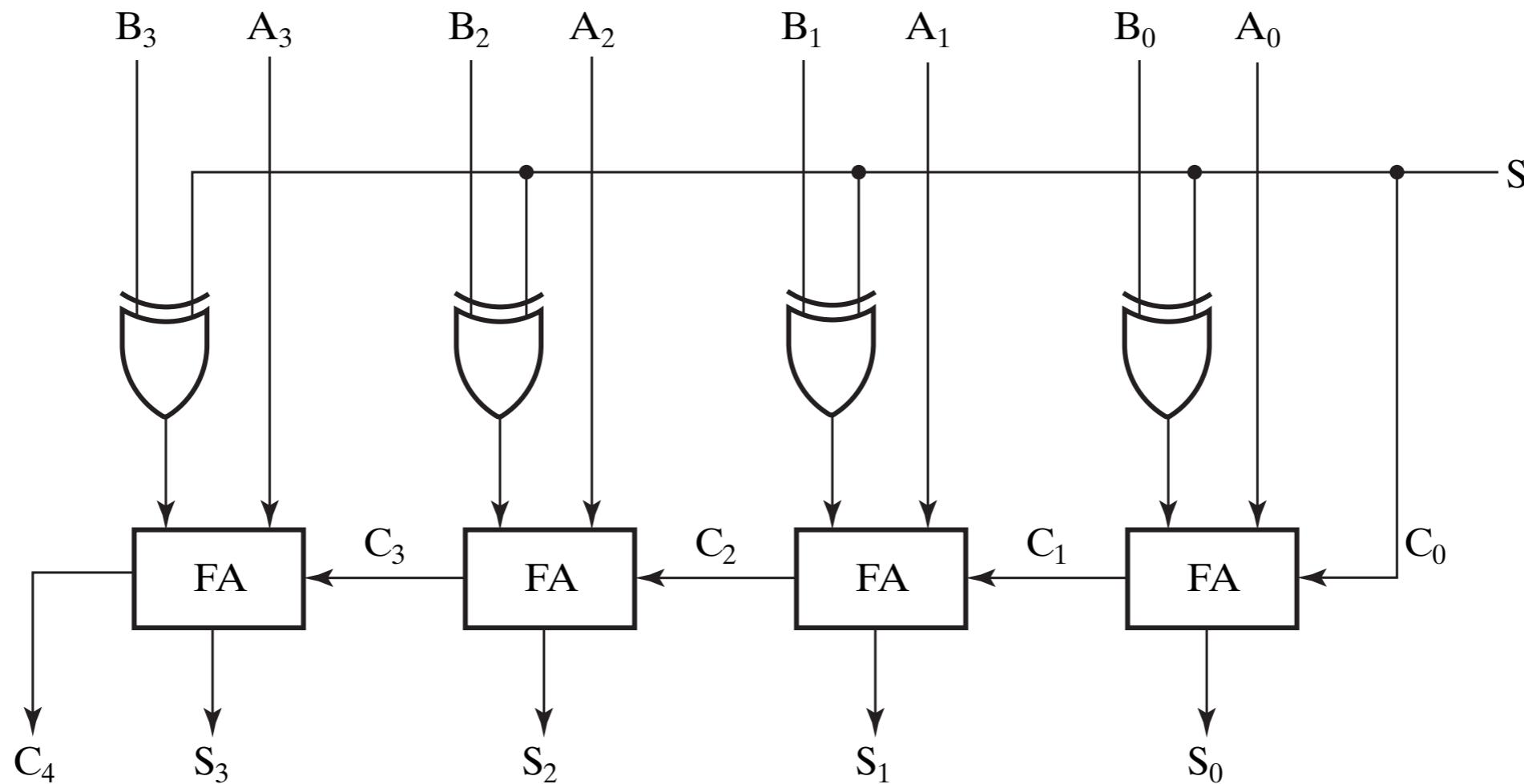

Handling overflow

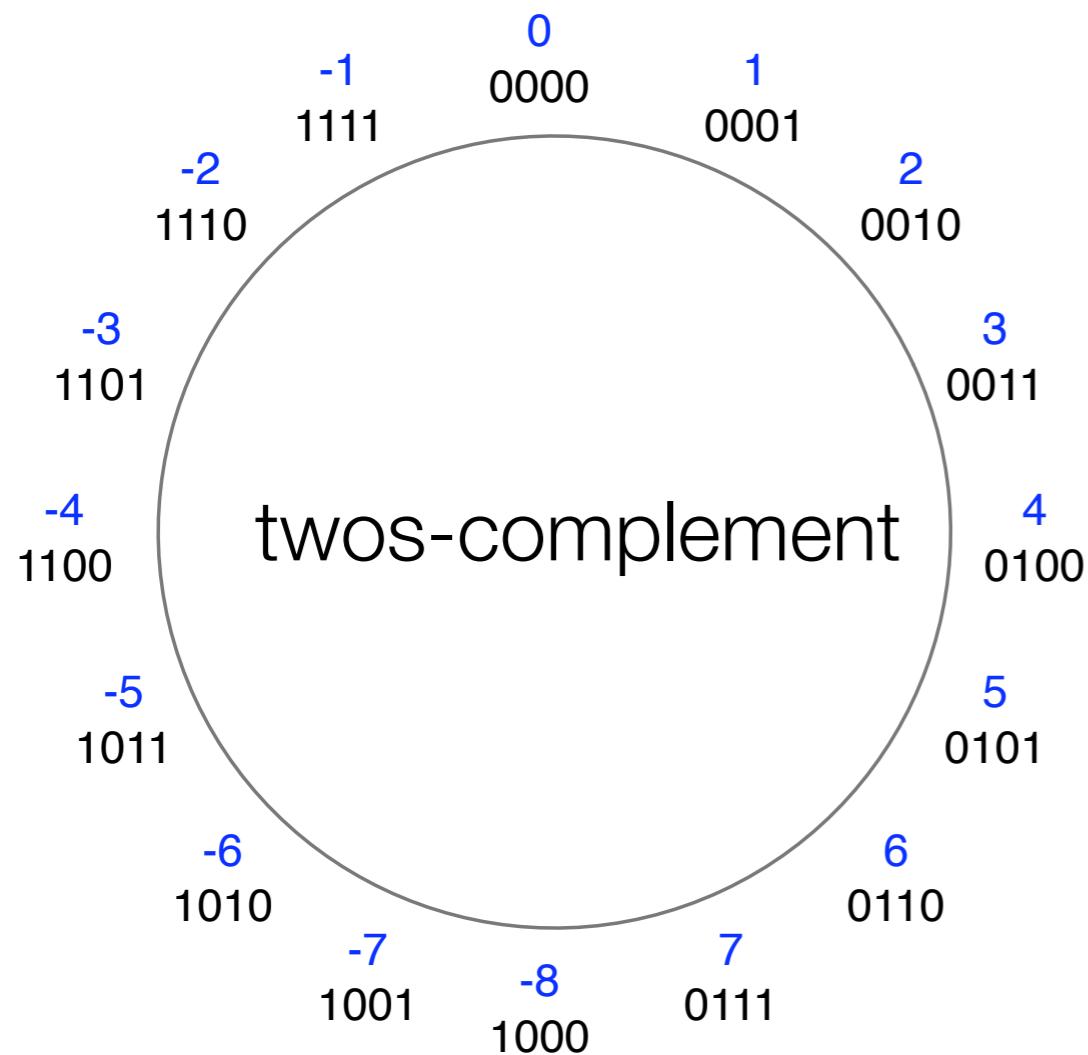

$$\begin{array}{r} 0111 \\ (5) \quad 0101 \\ (3) \quad \underline{0011} \\ 1000 \end{array} \quad (-8)$$


$$\begin{array}{r} 1111 \\ (-5) \quad 1011 \\ (-3) \quad \underline{1101} \\ 1000 \end{array} \quad (-8)$$

$$\begin{array}{r} 1000 \\ (-6) \quad 1010 \\ (-3) \quad \underline{1101} \\ 0111 \end{array} \quad (7)$$

$$\begin{array}{r} 0010 \\ (-6) \quad 1010 \\ (3) \quad \underline{0011} \\ 1101 \end{array} \quad (-3)$$

Handling overflow


c4	c3	c2	c1	c0
a3	a2	a1	a0	
b3	b2	b1	b0	
s3	s2	s1	s0	

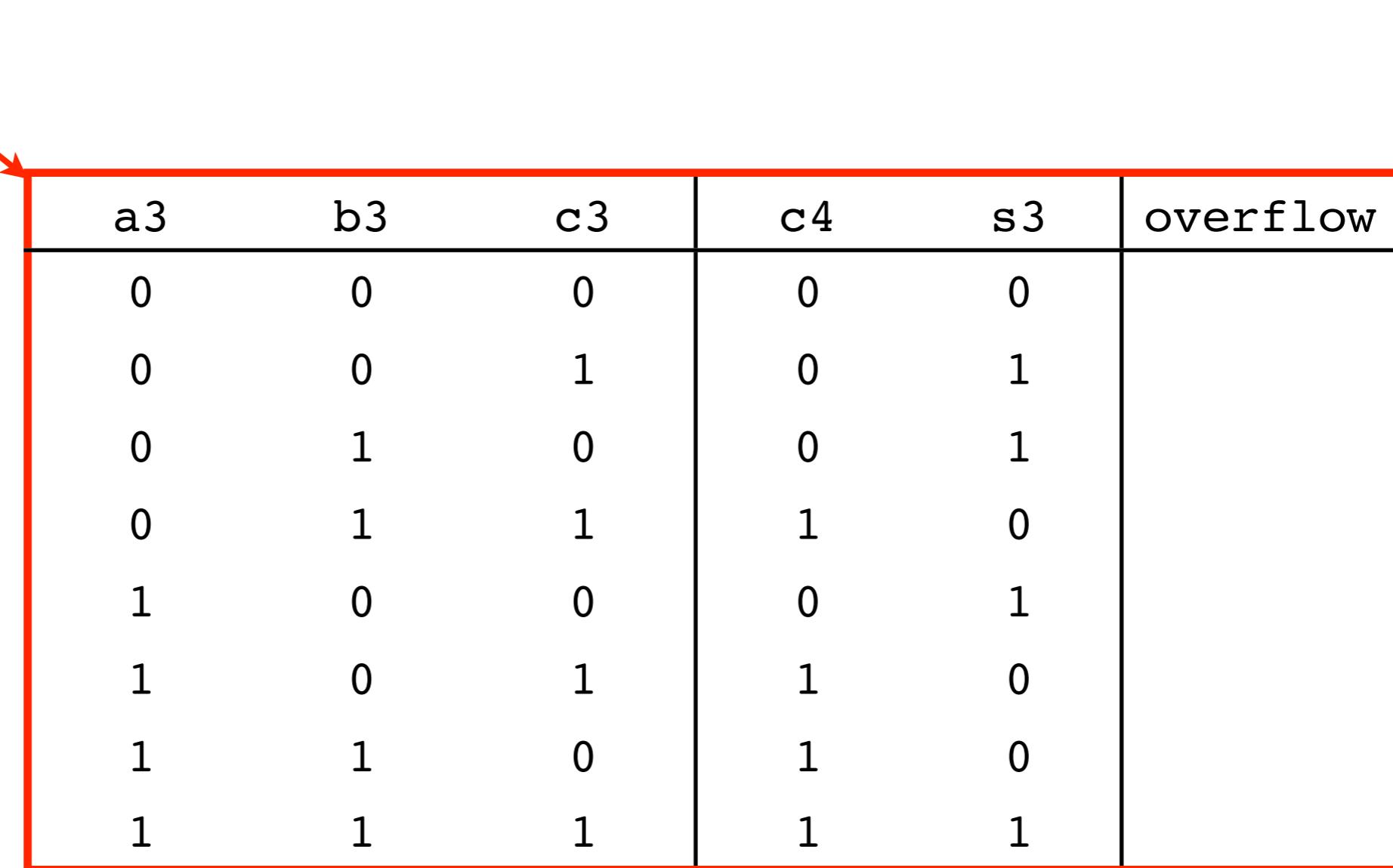

a3	b3	c3	c4	s3	overflow
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	


Overflow computation in adder/subtractor

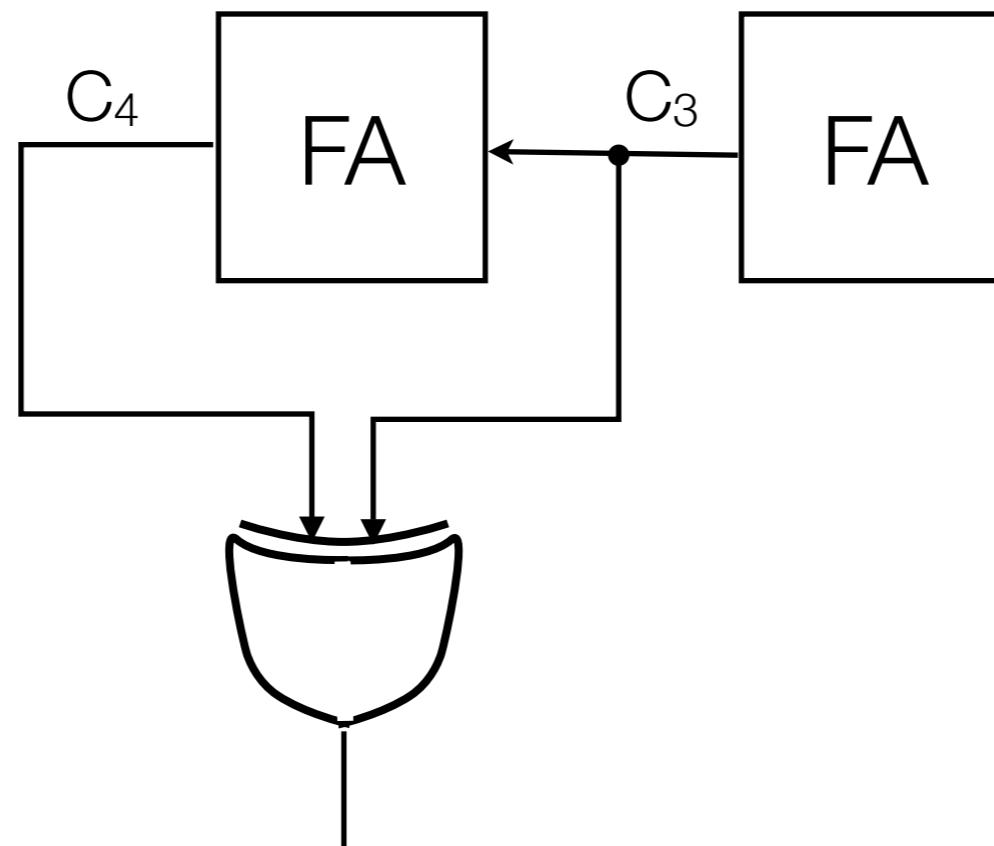For 2's complement, overflow if 2 most significant carries differ



Ripple carry adder delay analysis

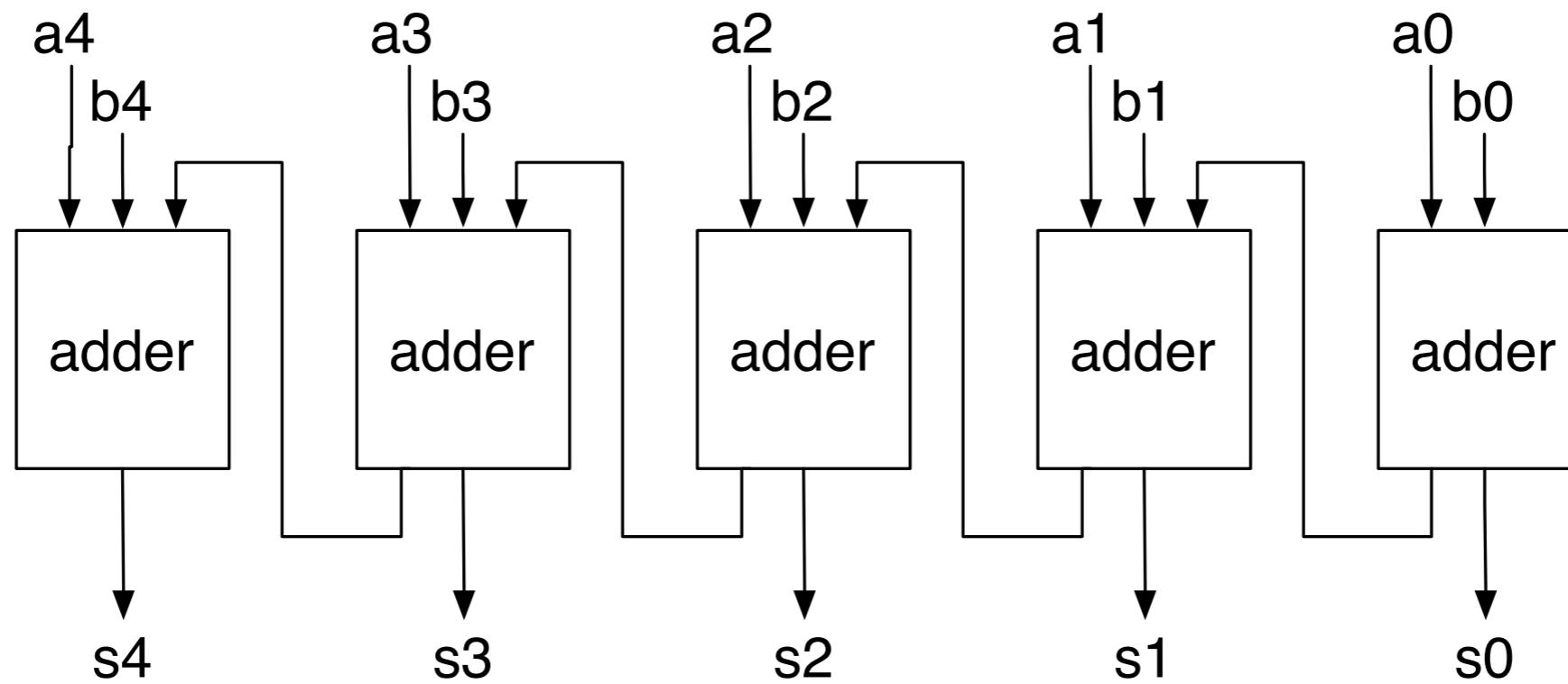- Assume unit delay for all gates
 - $S = A \oplus B \oplus Cin$
 - [S ready _____ units after A, B and Cin ready]
 - $Cout = AB + ACin + BCin$
 - [$Cout$ ready _____ units after A, B and Cin ready]



Carry lookahead adder (CLA)

- Goal: produce an adder of less circuit depth
- Start by rewriting the carry function

$$C_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$C_{i+1} = a_i b_i + c_i (a_i + b_i)$$

$$C_{i+1} = g_i + c_i (p_i)$$

carry generate

$$g_i = a_i b_i$$

carry propagate

$$p_i = a_i + b_i$$

Carry lookahead adder (CLA) (2)

- Can recursively define carries in terms of propagate and generate signals

$$C_1 = g_0 + C_0 p_0$$

$$C_2 = g_1 + C_1 p_1$$

$$= g_1 + (g_0 + C_0 p_0) p_1$$

$$= g_1 + g_0 p_1 + C_0 p_0 p_1$$

$$C_3 = g_2 + C_2 p_2$$

$$= g_2 + (g_1 + g_0 p_1 + C_0 p_0 p_1) p_2$$

$$= g_2 + g_1 p_2 + g_0 p_1 p_2 + C_0 p_0 p_1 p_2$$

- i th carry has $i+1$ product terms, the largest of which has $i+1$ literals
- If AND, OR gates can take unbounded inputs: total circuit depth is 2 (SoP form)
- If gates take 2 inputs, total circuit depth is $1 + \log_2 k$ for k -bit addition

Carry lookahead adder (CLA) (3)

$$C_0 = 0$$

$$C_1 = g_0 + C_0 p_0$$

$$C_2 = g_1 + g_0 p_1 + C_0 p_0 p_1$$

$$C_3 = g_2 + g_1 p_2 + g_0 p_1 p_2 + C_0 p_0 p_1 p_2$$

$$S_0 = a_0 \oplus b_0 \oplus C_0$$

$$S_1 = a_1 \oplus b_1 \oplus C_1$$

$$S_2 = a_2 \oplus b_2 \oplus C_2$$


$$S_3 = a_3 \oplus b_3 \oplus C_3$$

Contraction

Contraction is the simplification of a circuit through constant input values.

Contraction example: adder to incrementer

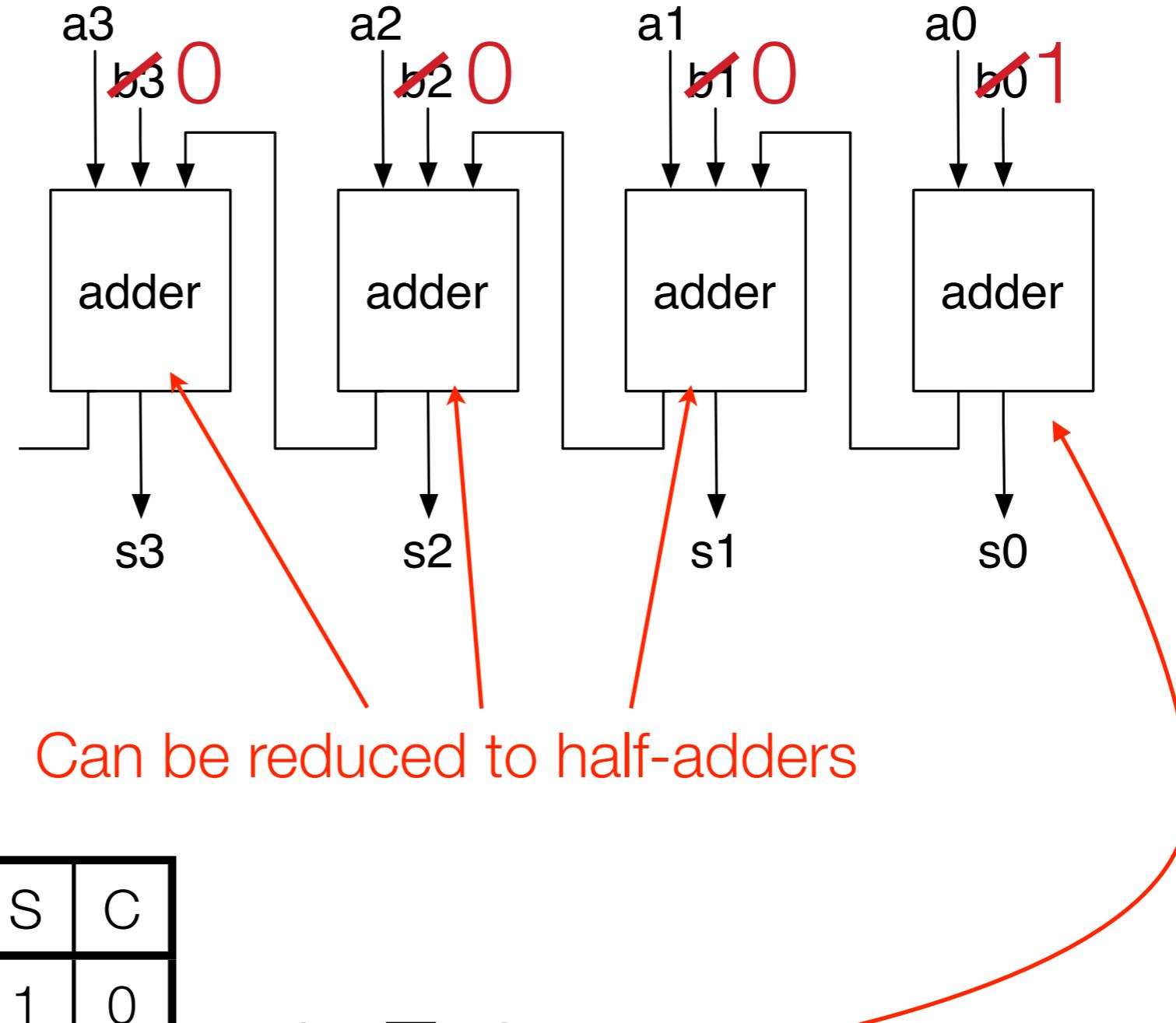- What is the hardware and delay savings of implementing an incrementer using contraction?




Incrementer
circuit

a_0	S	C
0	1	0
1	0	1

$$S_0 = \overline{a}_0, C_0 = a_0$$


Multi-wire notation

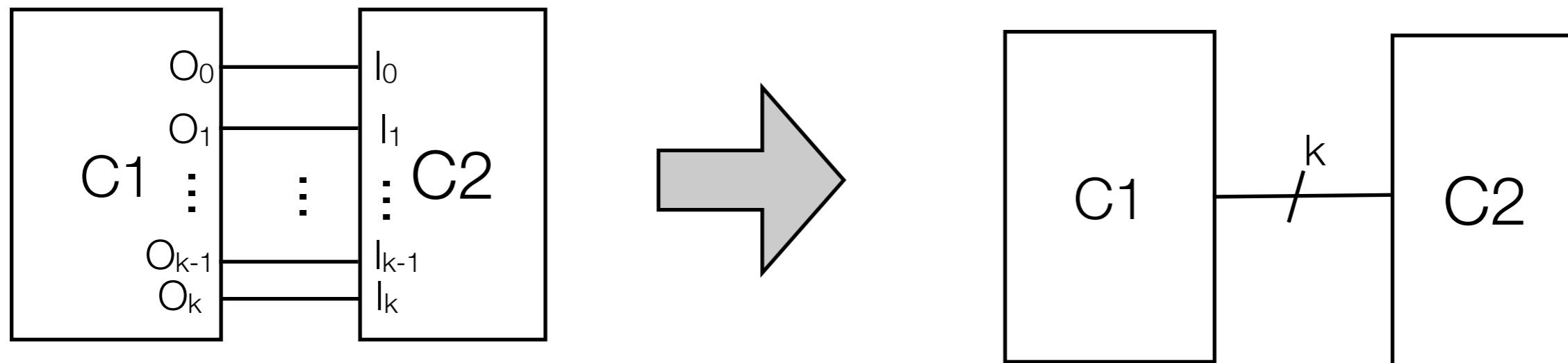- Useful when running a bunch of bits in parallel to the same (similar place)



Shifter Circuit

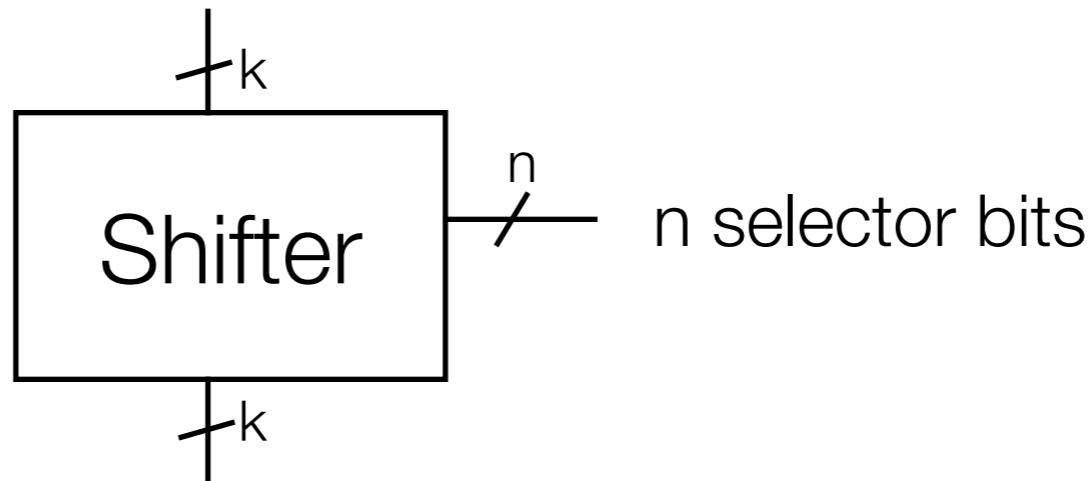- Shifts bits of a word: $A_{k-1}A_{k-2}\dots A_2A_1A_0$




$$B_{k-1}B_{k-2}\dots B_2B_1B_0$$

- Various types of shifters


- Barrel: selector bits indicate (in binary) how “far” bits shift
 - selector value = j , then $B_i = A_{i-j}$
 - bits can “wraparound” $B_i \pmod{2^n} = A_{i-j} \pmod{2^n}$ or rollout ($B_i=0$ for $i < j$)
- L/R with enable: $n=2$, high bit enables, low bit indicates direction (e.g., 0=left [$B_i = A_{i-1}$], 1=right [$B_i = A_{i+1}$])

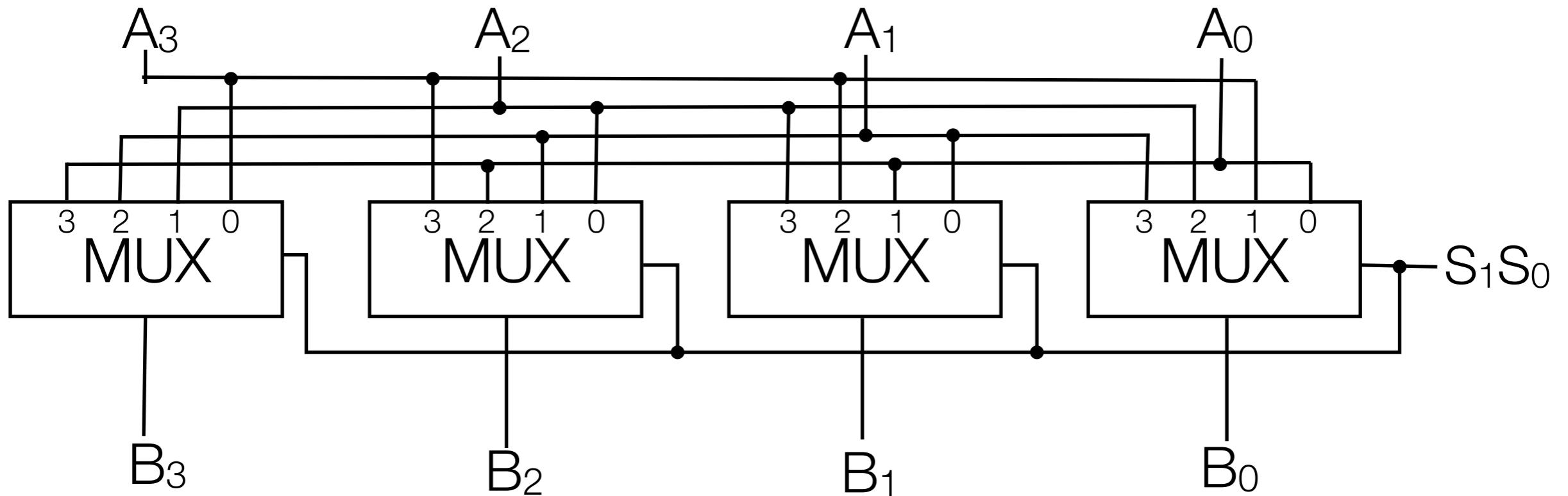Barrel Shifter Design with wraparound (using MUXes)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$

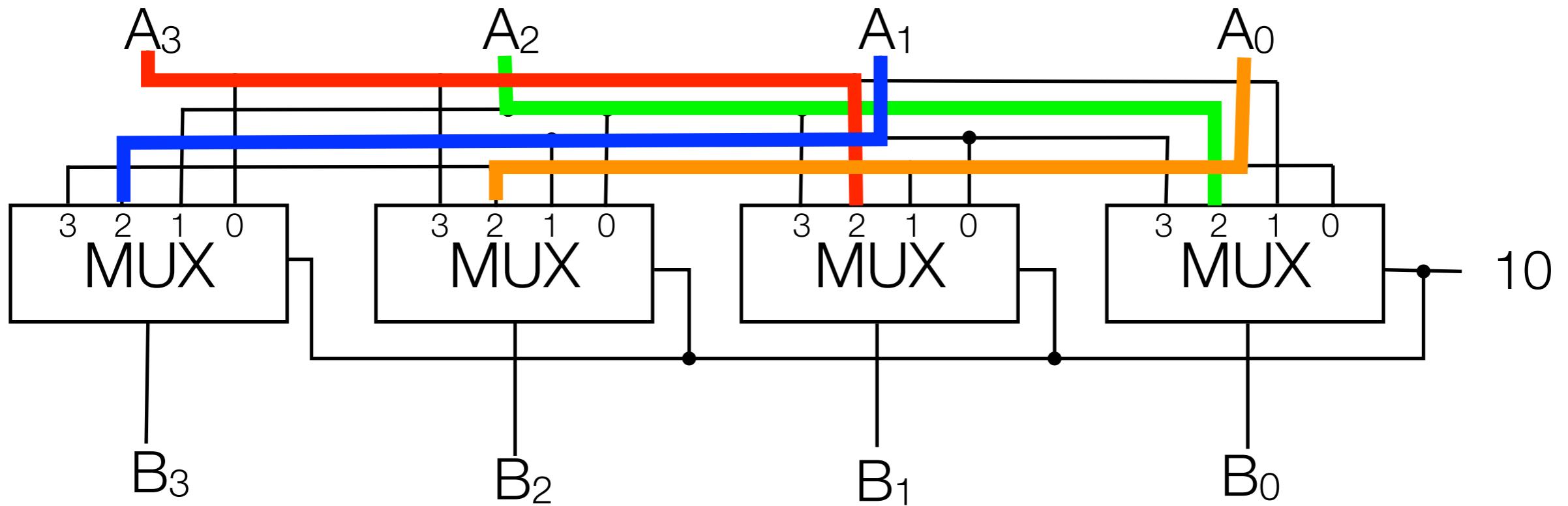Barrel Shifter Design with wraparound (using MUXs)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$
- Selector is 10 (i.e., 2 binary): each MUX entry 2 is selected

L/R Shift w/ Rollout

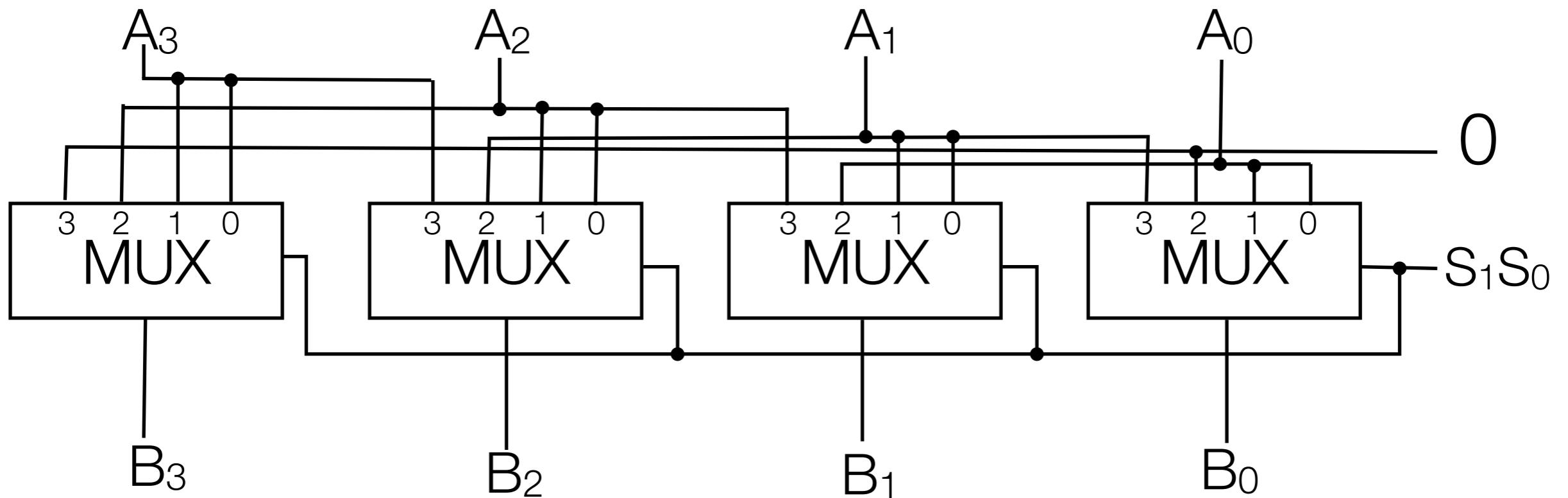

- Basic form of design:
 - 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
 - 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
 - Note 0 feeds (0's roll in when bits rollout)

L/R Shift w/ Rollout

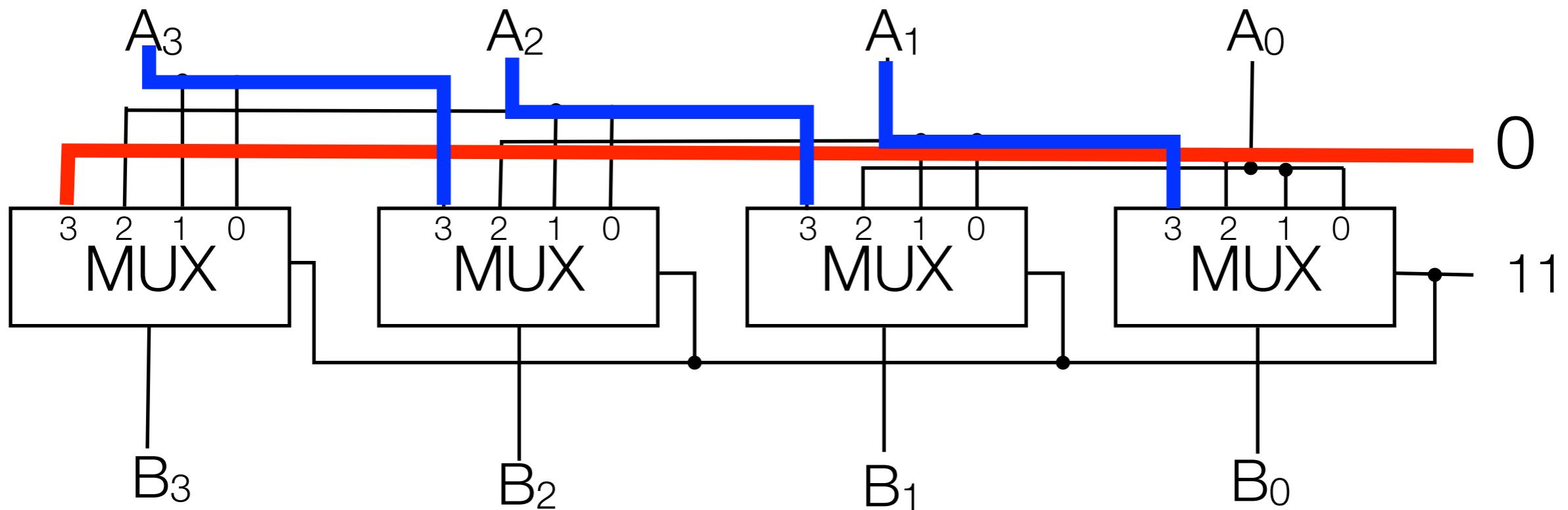

- Basic form of design:
 - 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
 - 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
 - Note 0 feeds (0's roll in when bits rollout)